

# Hardware considerations Electric Power Steering

EPS Workshop China



# Power on Demand Electric Power Steering



- Demand oriented torque controlled electric motor
- Reduced Average Power Consumption down to < 50W



**Total Equivalent Electric Power Saving ~ 250 W**



Source : ZFLS




Continuously Mechanical Hydraulic Pump

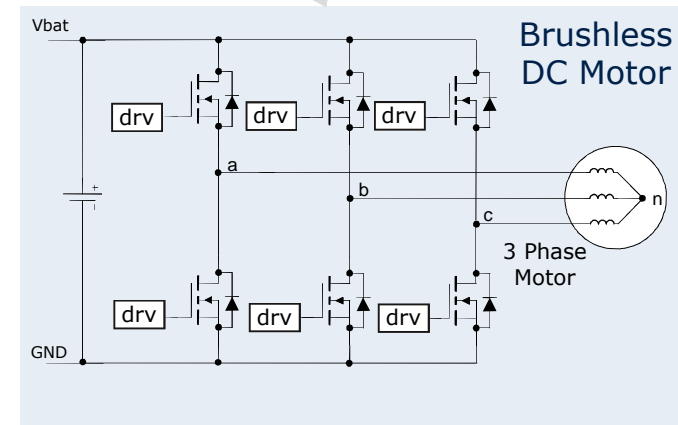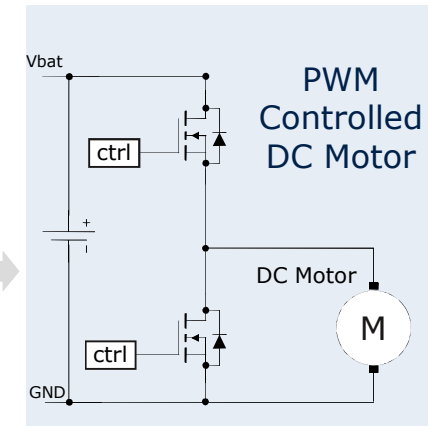

**CO<sub>2</sub>-reduction ~ 5.9 g/km**

# Electric Power Steering System

## Focus of this session

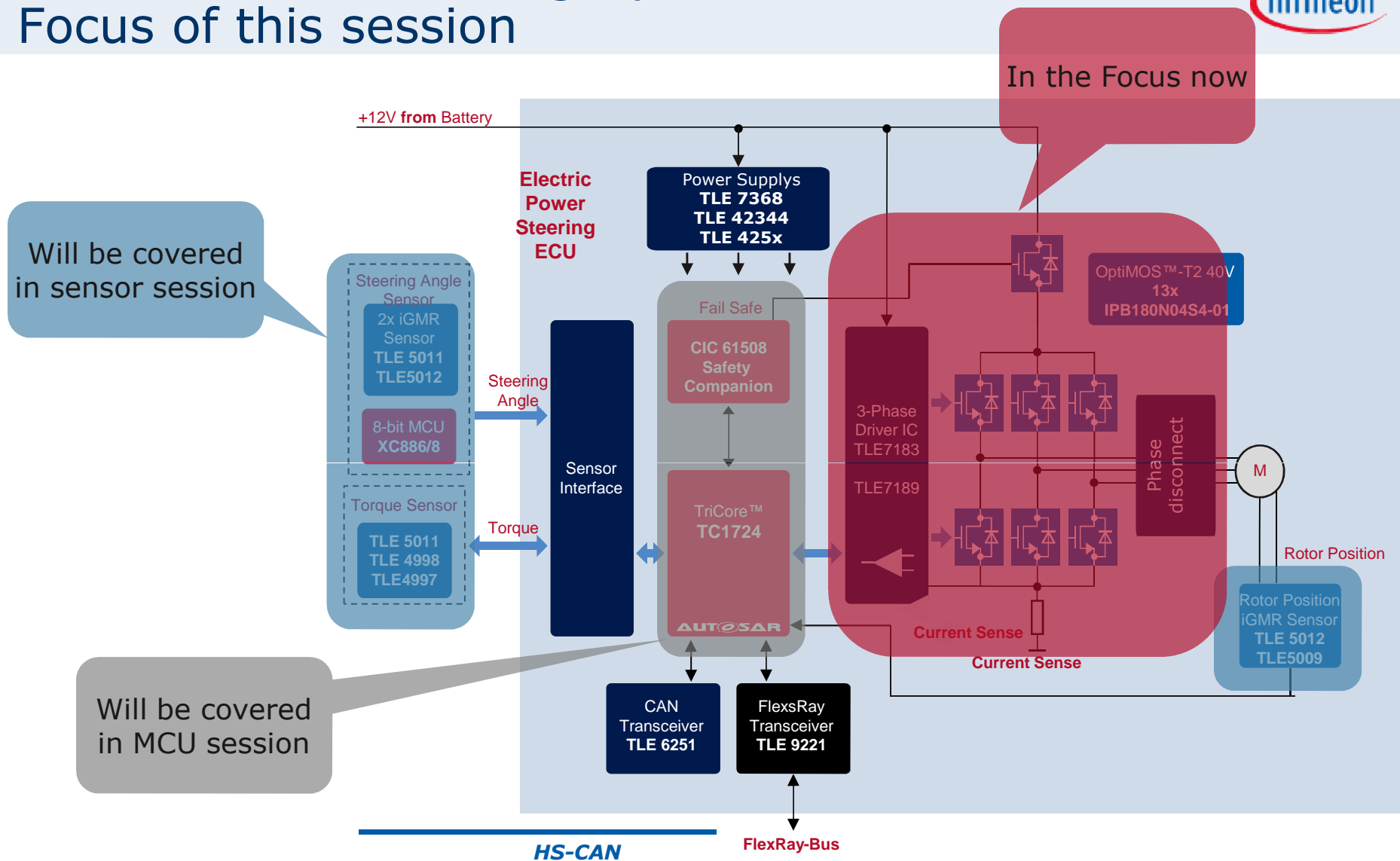

# Application requirements Power Steering

## ■ Basic requirements to power stage

- 3-phase motor drive
- 100-160A phase current
- Field oriented control
- mostly 12V application
- High functional safety

Drive high  
currents

Measure current  
precise

Second  
switch-off path

## ■ Trends

- has to work at lower supply voltages
- (only one shunt for current measurement)
- increasing accuracy of current measurement
- highest efficient usage of motor (0...100% duty cycle)
- fulfill ASIL D safety requirement in application

# Agenda

## ■ Application requirements EPS (Permanent Magnet Synchronous Motor)

### ■ Driving high currents

- ☐ Spikes: Why they are harmful
- ☐ Layout recommendations
- ☐ Requirements to MOSFETs and Driver ICs


### ■ Measure Current precisely

- ☐ How many shunts to use?
- ☐ How does it work with one shunt
- ☐ Requirements for driver IC
- ☐ What to consider with IFX OpAmps in driver ICs


### ■ Functional Safety: Second switch off path

- ☐ Star-Point relay vs. MOSFETs


# Basic function of each Power Bridge

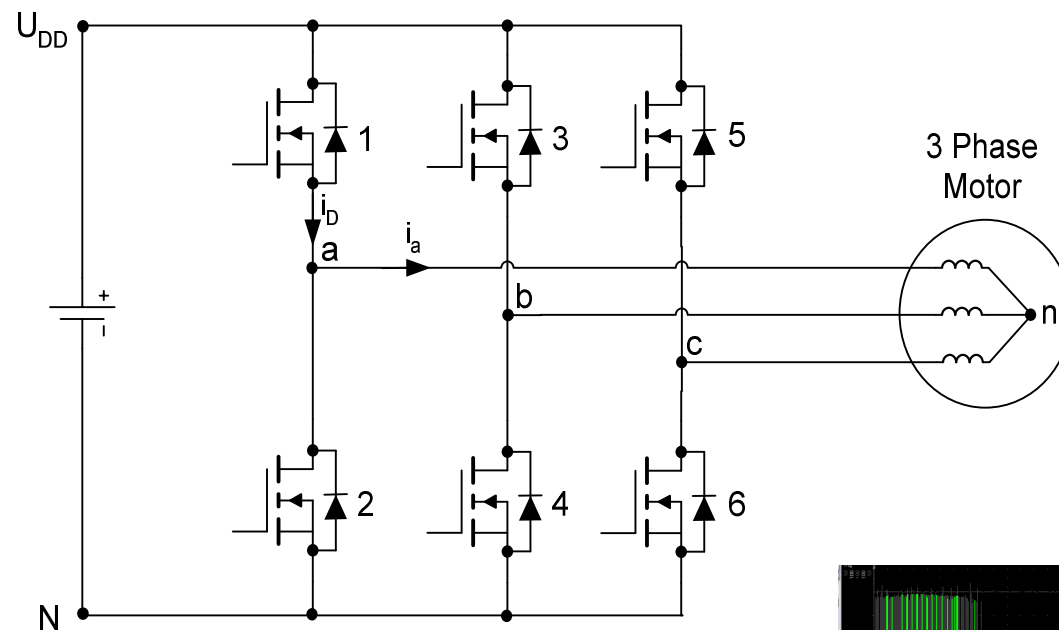

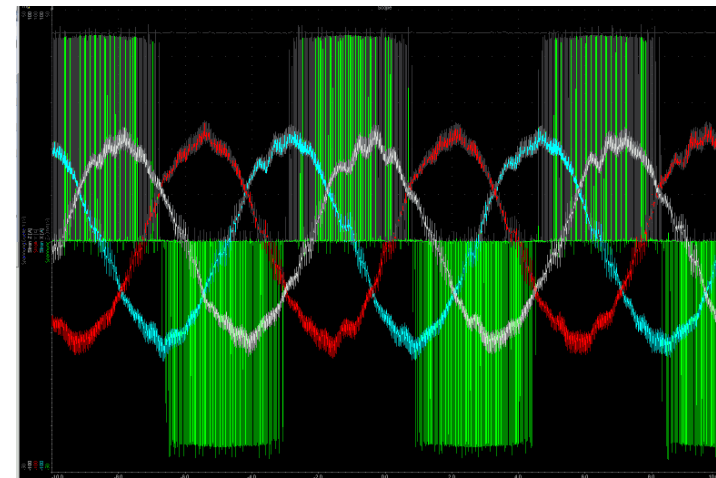- **Task of the bridge**
  - Switch voltage at phase
  - Let current commute
    - Current jumps from LS to HS MOSFET and vice versa




# Example MOSFET 1 and 2 switching

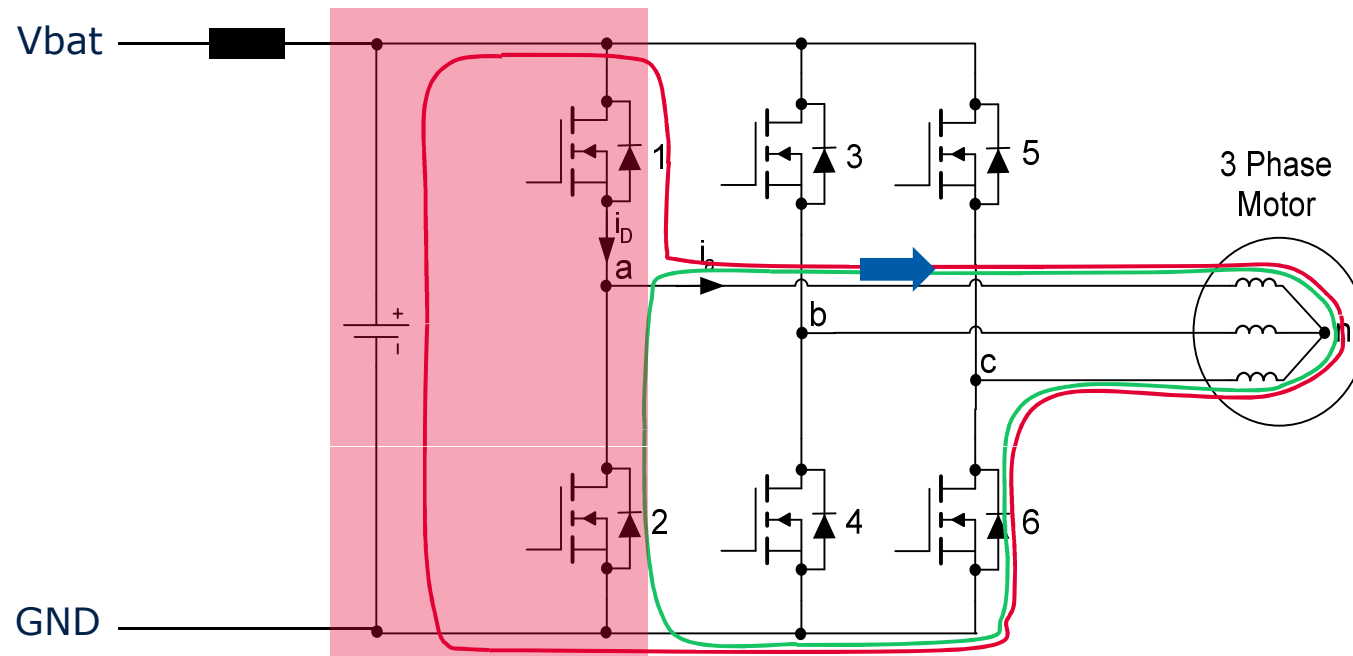

- Example: MOSFET 1 and 6 on
- Switch off 1: Current flow changes
- Current will be freewheeling in Diode of MOSFET 2

# Example MOSFET 1 and 2 switching

## Current shape

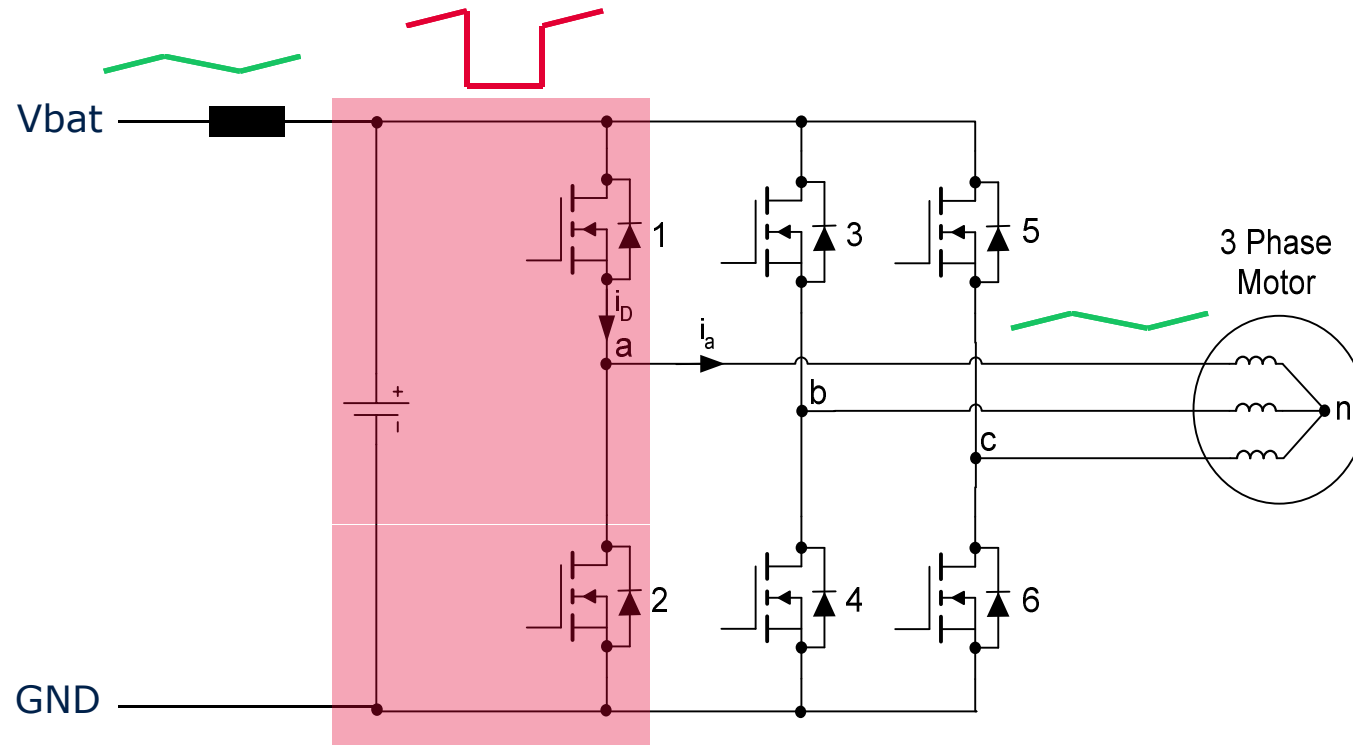


- Current from battery smoothened by inductance of  $\Pi$ -filter ( $\sim \mu\text{H}$ )
  - $\sim 1\text{A}/\mu\text{s}$
- Current in Motor smoothened by motor inductance ( $\sim 50\mu\text{H}$ )
  - $\sim 0,2\text{ A}/\mu\text{s}$
- Current in marked area jumps from 0 to motor current
  - $\sim 1000\text{A}/\mu\text{s}$
  - 10 nH together with  $1000\text{A}/\mu\text{s}$  are creating 10V Spikes



# Why are voltage spikes critical?

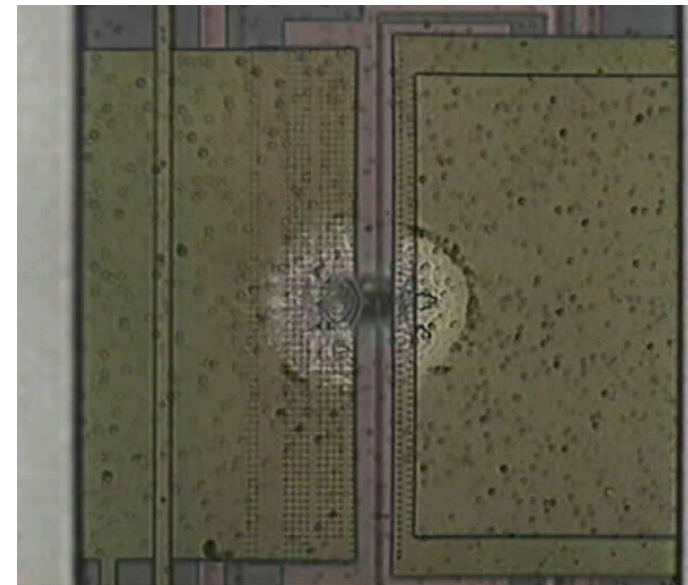- Examples for Problems in Motor drives:
  - Unwanted Short circuit detection (noise)
  - Violation of maximum ratings of the components
  - Electro-magnetic noise
  
- Consequences
  - Motor does not run reliably
  - Destruction of components
  - Disturbance of analog signals
  - EMC Problems




# Over and under voltages Spikes caused by Stray Inductances

Commutations means generating  $di/dt$  in the „red path“

$L$  is the sum of the inductances in the red path.

$U$  is generated by switching off a MOSFET

$$\frac{dI}{dt} = -\frac{U}{L}$$

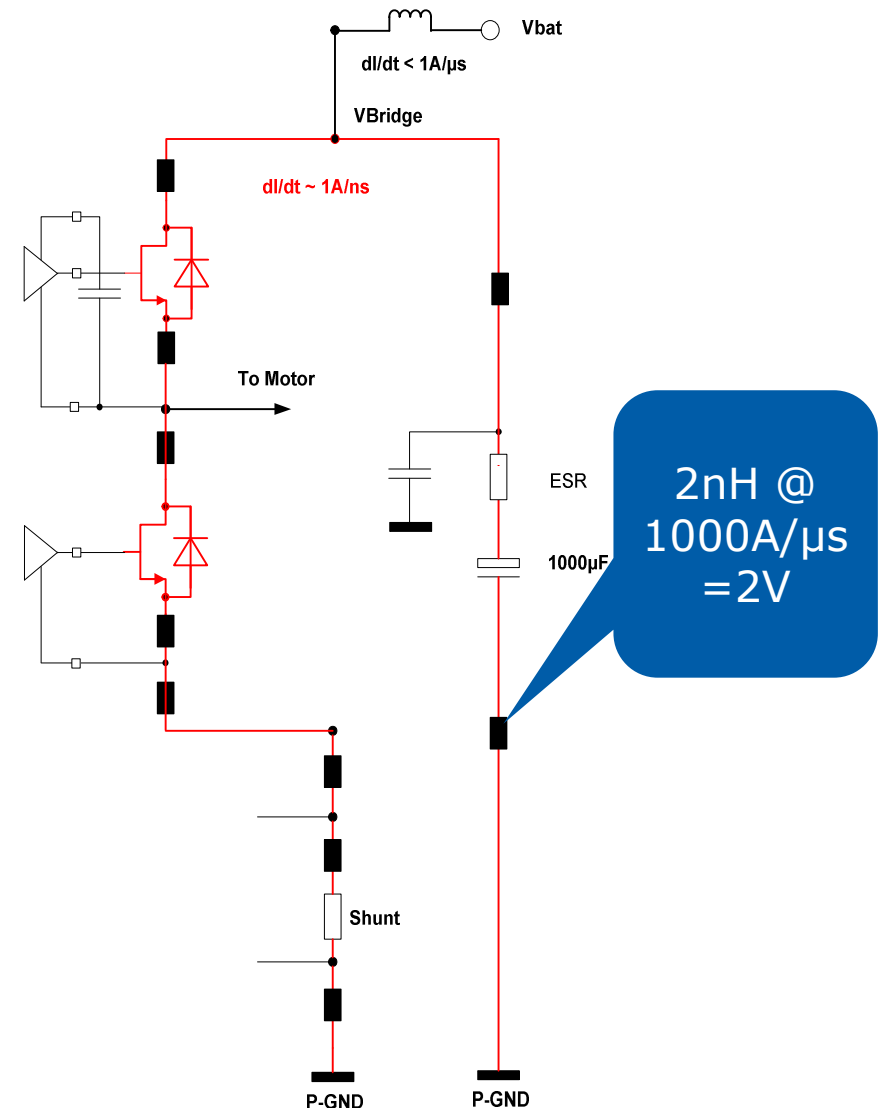

# Over and under voltages Spikes caused by Stray Inductances

## Example 1:


- 1) Current flows from motor to LS switch
- 2) LS switch is switched off
- 3) Current flows over diode of HS switch

Voltages in red are related to GND  
Voltages in black are relative voltages

**di/dt across stray inductances cause:**

- Over and under voltages
- EMC noise
- ... result in high component costs


→ keep stray inductances small !!!

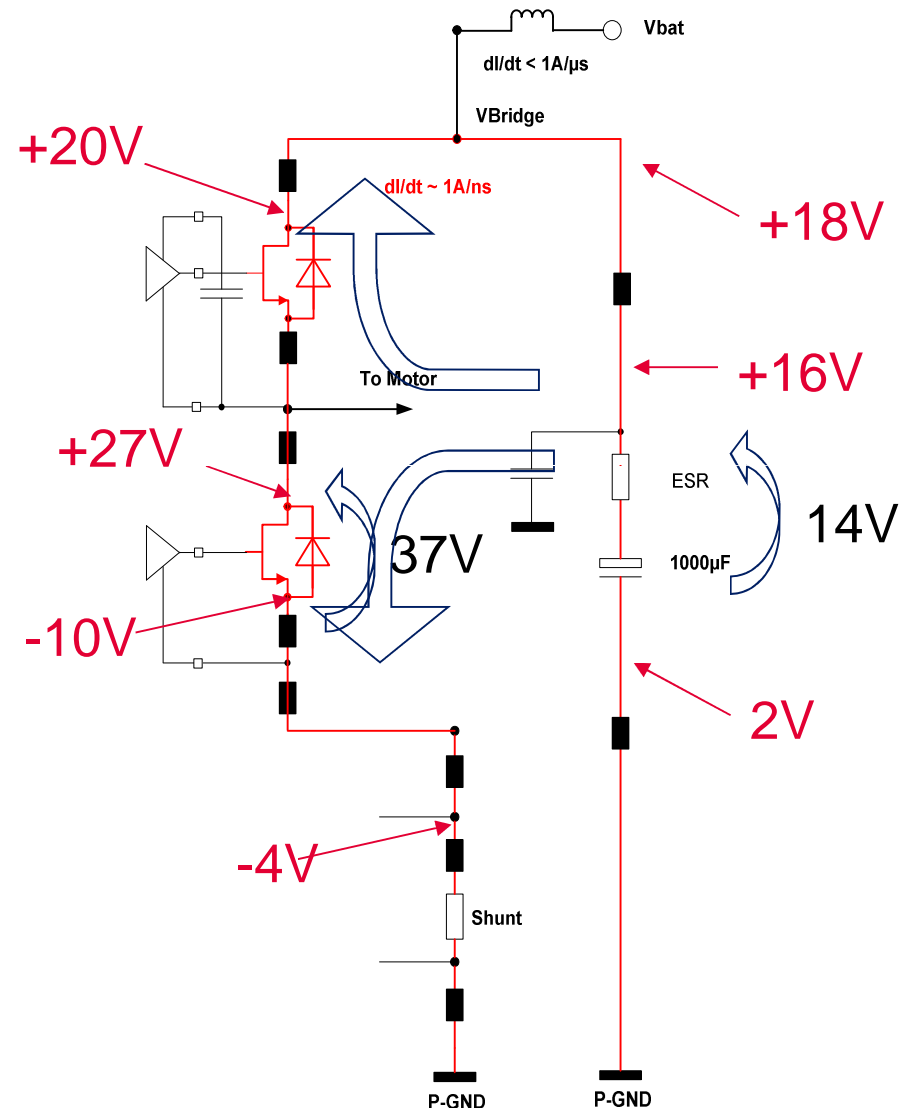

# Over and under voltages Spikes caused by Stray Inductances

## Example 2:

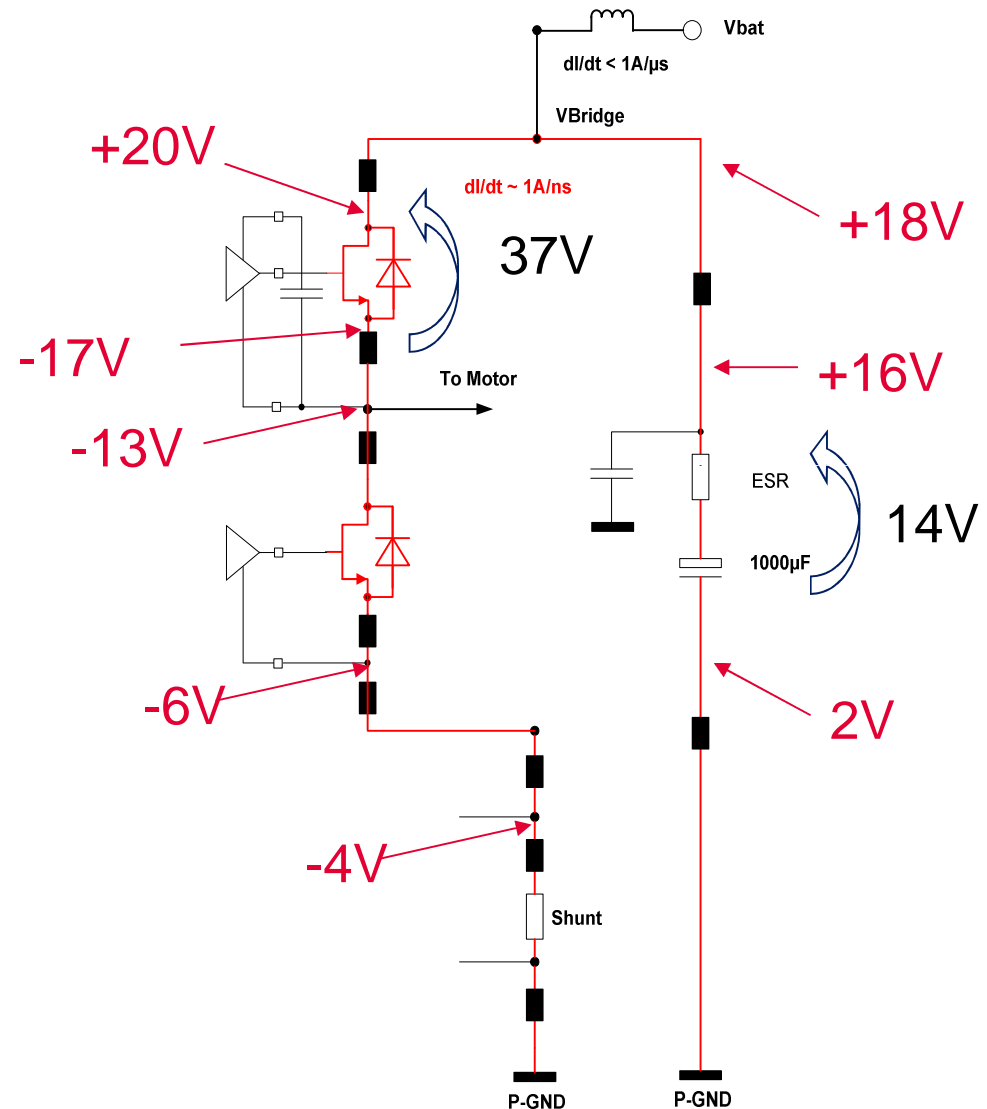- 1) Current flows from motor to HS switch
- 2) HS switch is switched off
- 3) Current flows over diode of LS switch




# Over and under voltages Spikes caused by Stray Inductances



- How to identify stray inductivities
  - Find out the current path on the PCB
  - Investigate the Area which is created by this path

→ Not so good

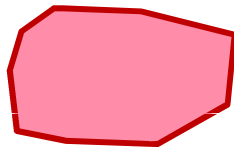

→ better



- The smaller the area – the better
  - No long distances !!

# What can be done to avoid stray inductivities?



- Place all components in the red area close together

- HS + LS MOSFET

- DC Link capacitor (Elko + ceramic cap)

- Shunt

- Avoid thin connections

- Parallel wires have lower inductance as a single wire



- If possible:



- Optimize each half-bridge for itself

- One cap per half-bridge needed

# Reducing stray inductances and ohmic resistances
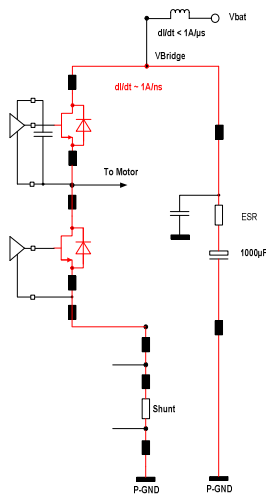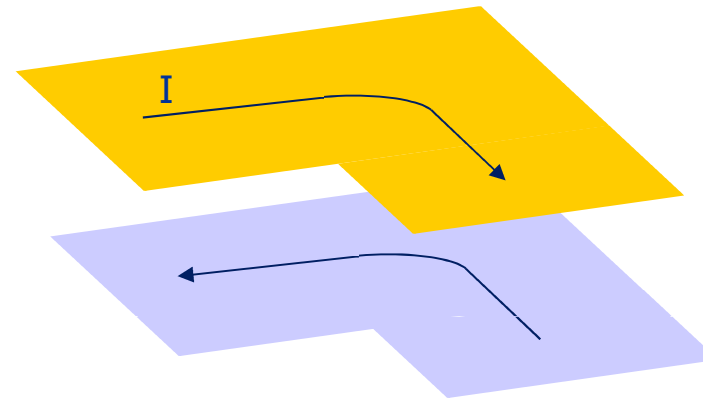
## More possibilities

- Use of GND and VBB planes
- “guided” current flow





**Generated electro-magnetic field compensate  
in some distance**

**Planes add “capacitance” all over the current path =  
smoothen over and under voltages**

# Reducing stray inductances and ohmic resistances
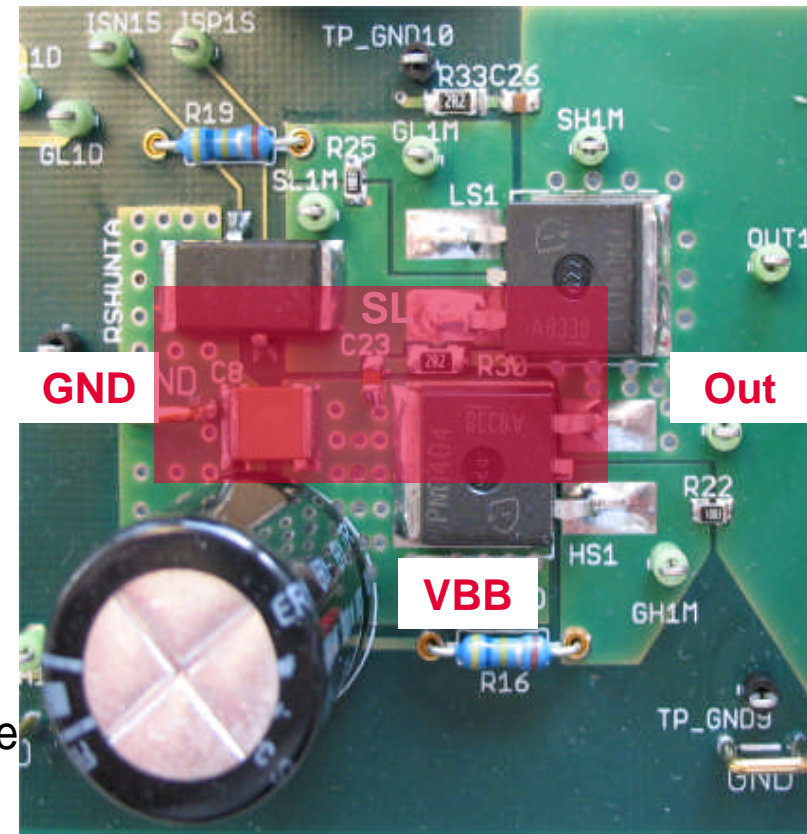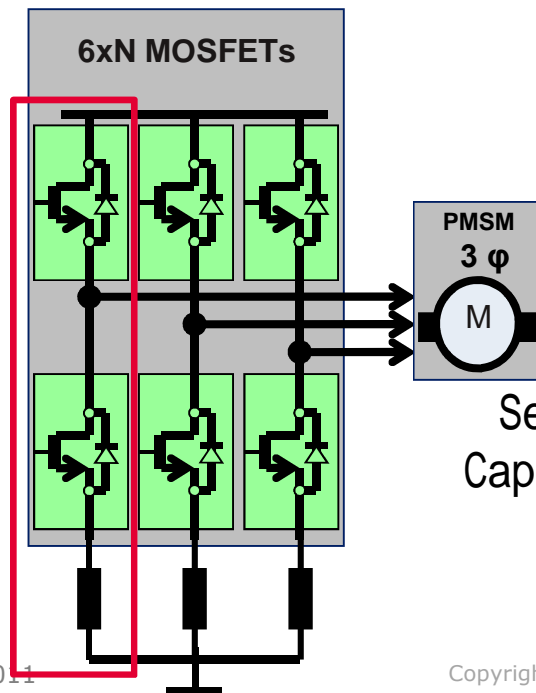
## Example 1: Optimized Half Bridge = 3 shunts

- Minimize the distances in the red path
- Use LOW ESR / low ESL capacitors
- Avoid vias (resistance)







# Reducing stray inductances and ohmic resistances
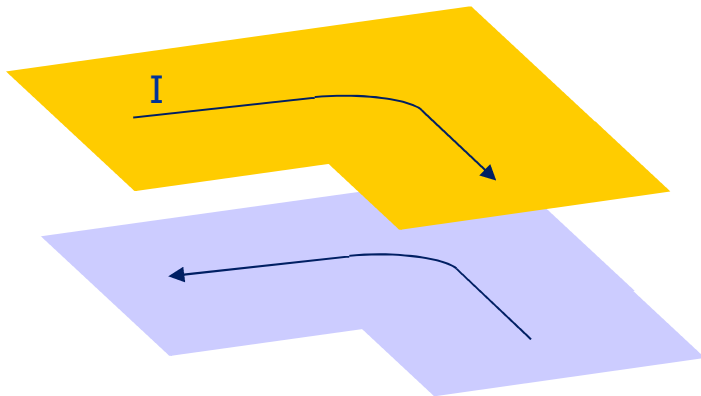
## Example with common shunt

- Use of GND and VBB planes
- Current flows back from shunt to capacitor through GND plane




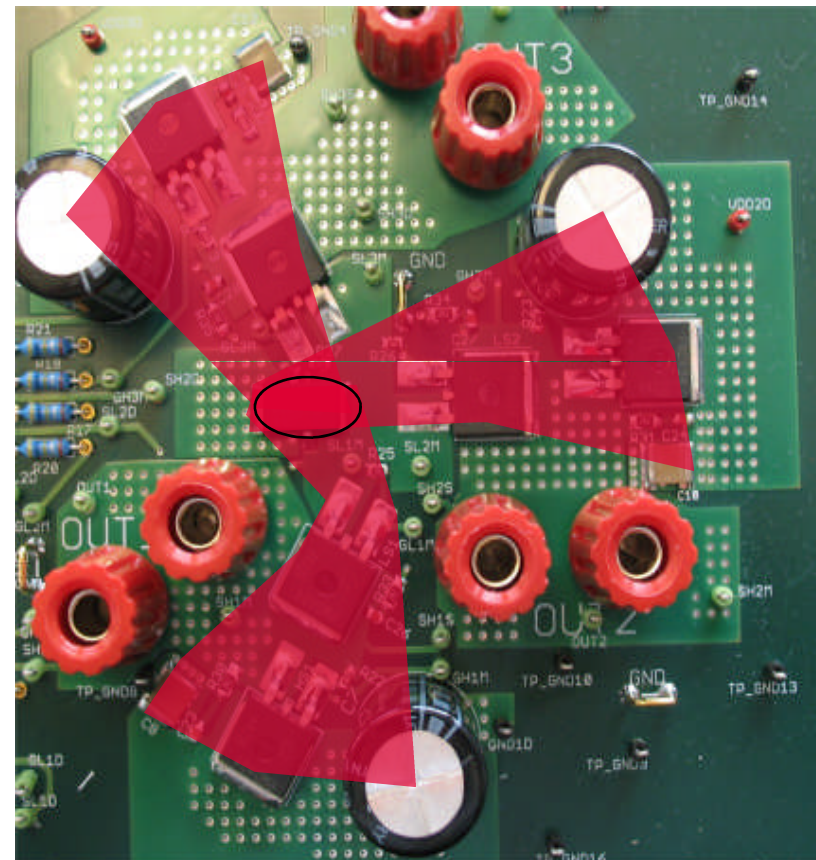**GND and VBB planes are good heat sinks as well !**




# Further noise reduction

## Some possibilities

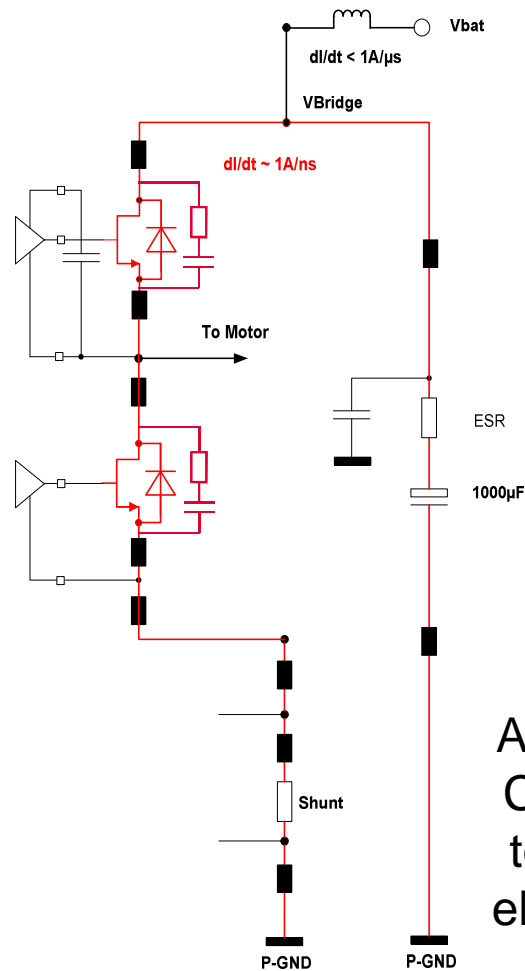


Add a snubber circuit to each MOSFET

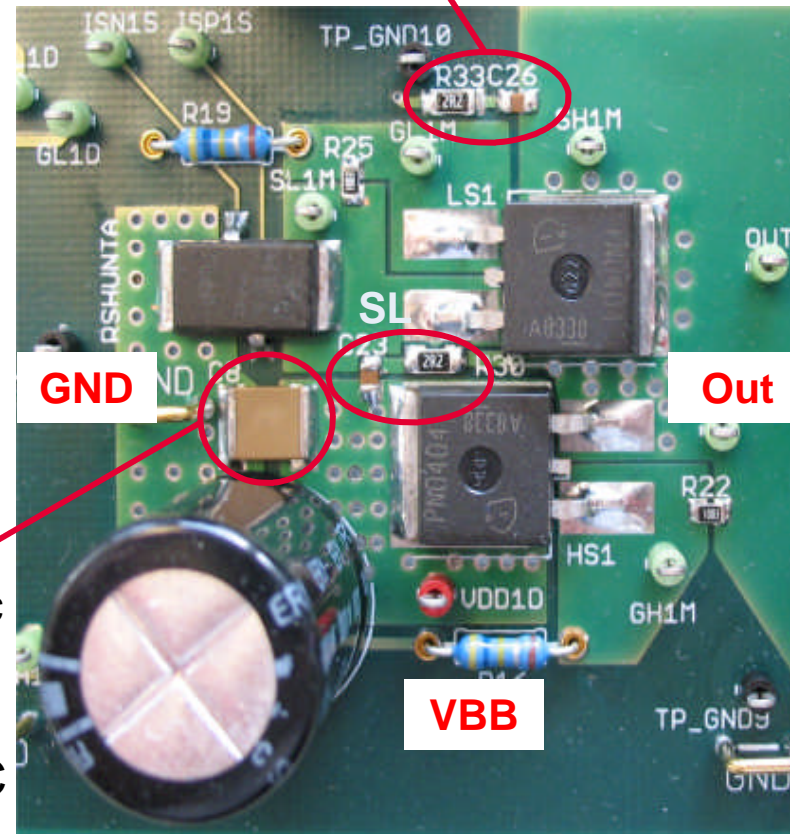

Add ceramic C in parallel to the large electrolytic C

# The Seven Deadly Sins

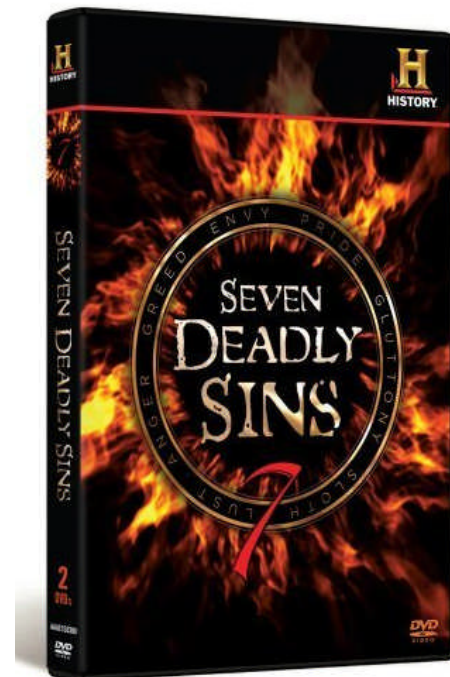1. Place MOSFETs far from each other
2. Use Elko with high ESR and ESL
3. Forget to place ceramic caps in parallel
4. Place Elko or ceramic cap far from MOSFETs
5. Use thin connections
6. Forget that shunt is part of the critical path
7. Optimize the wrong paths (battery or motor connection)



# Additional effects leading to over and under voltages:



- **Stray inductances**  
Over and under voltages ( $L \times di/dt$ )  
Power dissipation
- **Ohmic parasitics**  
Over and under voltages  
Power dissipation
- **Snappy diodes of MOSFETs**  
High  $dI/dt$   
Over and under voltages  
EMC noise




**Normally OK**

## Choice of MOSFETs


- **Use MOSFETs with a soft recovery behavior (not snappy)**
- **Problem: Specifications of MOSFETs do not provide this information (Qrr and trr are only indications)**
- **Proposal: Test your choice of MOSFETs in EMC tests to see the difference**
- **IFX MOSFETs (OptiMOS™-T) get usually good feedback !**
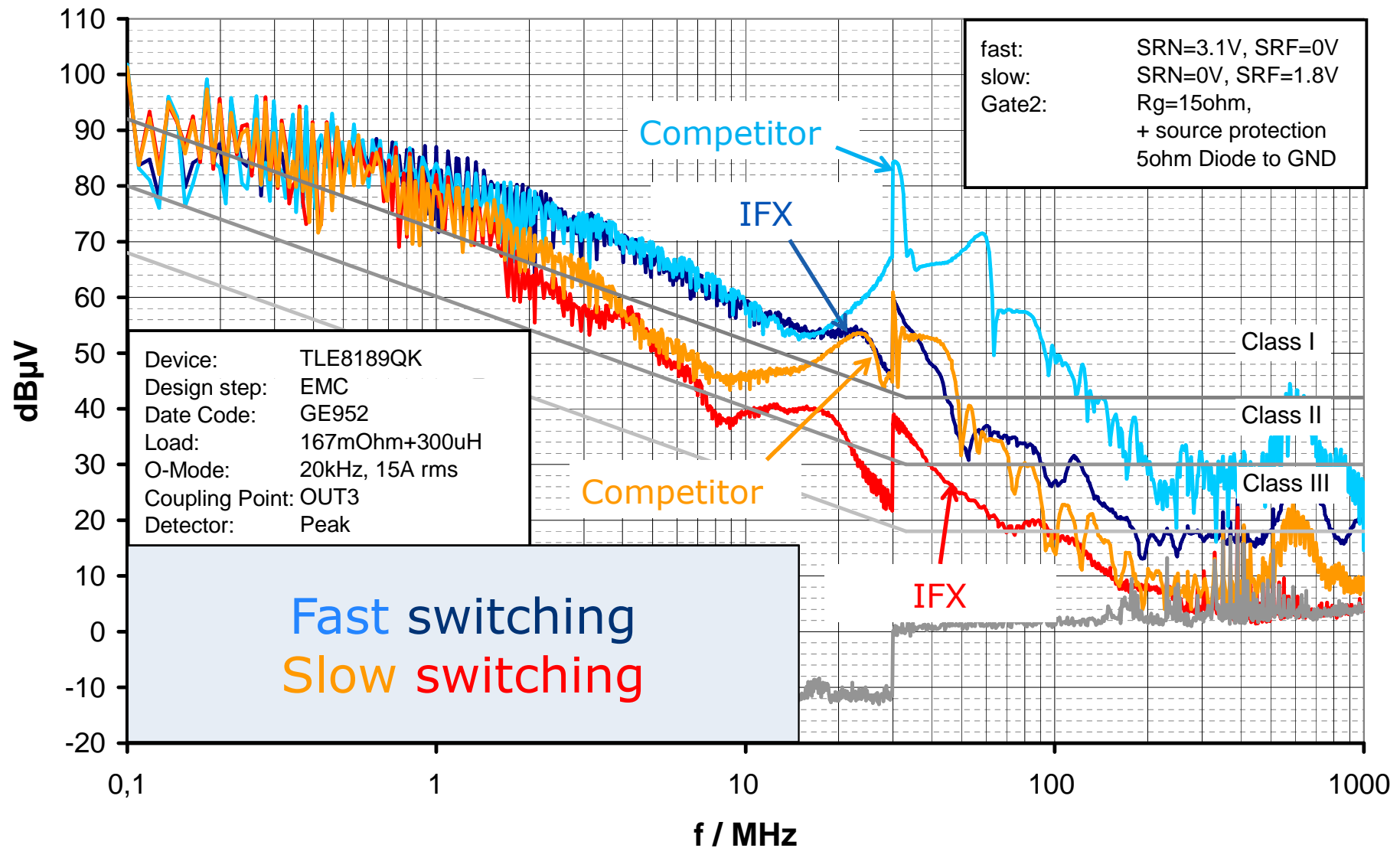
# EMC characteristics results comparison OptiMOS™-T2 MOSFET vs competitor


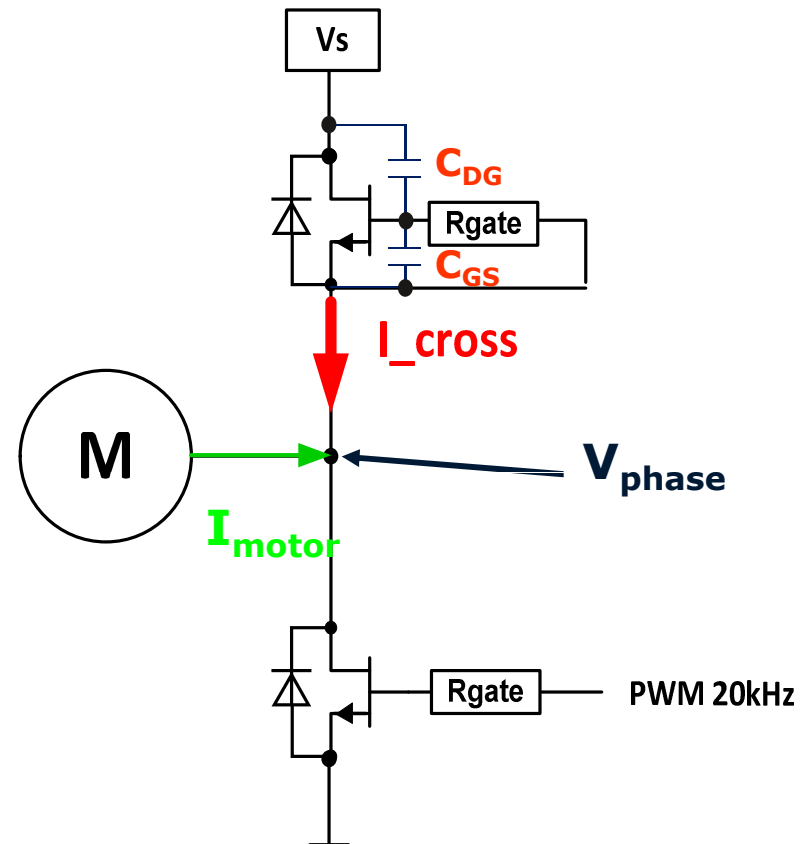
# Cross Current in MOSFET Inverter


- PWM in an MOSFET inverter
  - Low side MOSFET is switched ON  $\rightarrow$  VDS of HS2 rises fast
  - $C_{DG}$  and  $C_{GS}$  act as capacitive voltage divider
  - Rising VGS caused by  $C_{DG}$  and  $C_{GS}$
  - High side MOSFET switches "on" a bit
  - $I_{cross}$  might flow


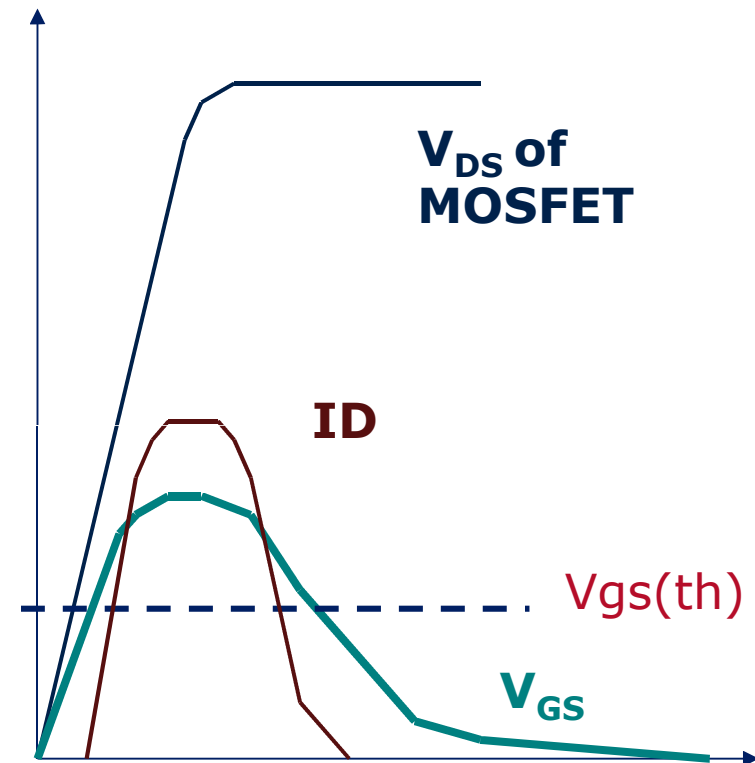
# Cross Current in MOSFET Inverter

$$V_{GS} \approx \left( \frac{C_{GS}}{C_{GD}} \right) V_{DS}$$

- If  $V_{GS}$  exceeds  $V_{GS(th)}$  → current will flow across the entire bridge leg → Cross Current
- The higher  $C_{GS} / C_{DG}$  the less cross current
- $C_{GS} / C_{DG}$  of OptiMOS™-T2 is 8x higher than competition






## ■ 160A B6-Bridge

- Between 1-2mOhm MOSFET
- 40V Normal Level ( $V_{gs(th)} > 2.5V$ )
- high current rating package
- Low gate charge
- automotive qualified
- Low feedback of VDS to VGS



**IPB180N04S3-02 or IPB180N04-00**

e.g.	IPB180N04-00	
RDson	0,98mΩ max @ RT	
Idrain	180A	720A peak !!
RthJC	0,5 K/W	good cooling
Qgtot	220 nC	low gate charge
Qgd	29 nC	low feedback to gate!
Qrr	132nC	good EMC behavior

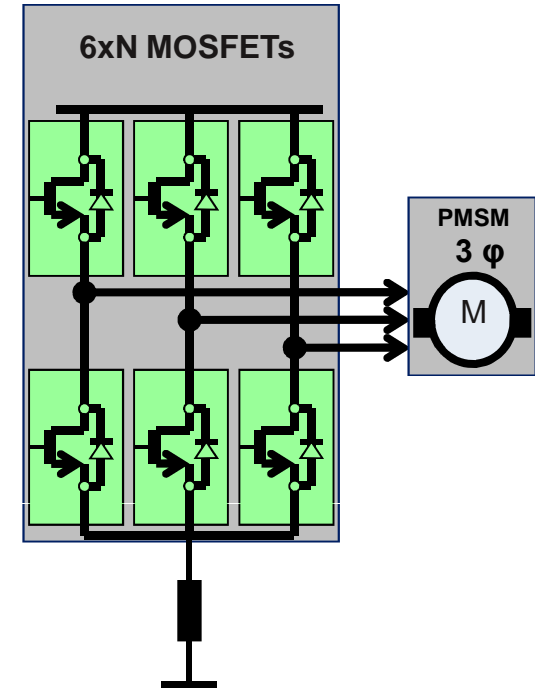


# Application requirements Power Steering

## ■ 160A B6-Bridge -> Diver Requirements


- powerful output stage up to 1.5A
- Robust to positive and negative spikes +/- 7V at SL
- Separate Source connections 4
- Floating output stages 4





**TLE7183 / 89 / 85 / 84**

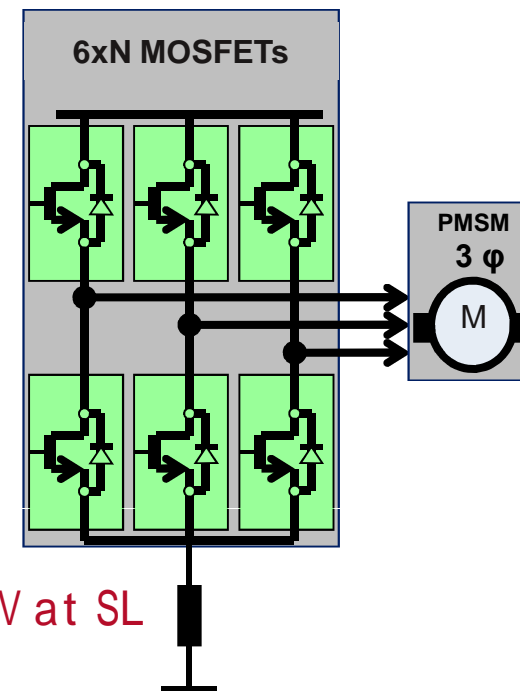

# TLE7183 3-Phase Driver IC for 12V

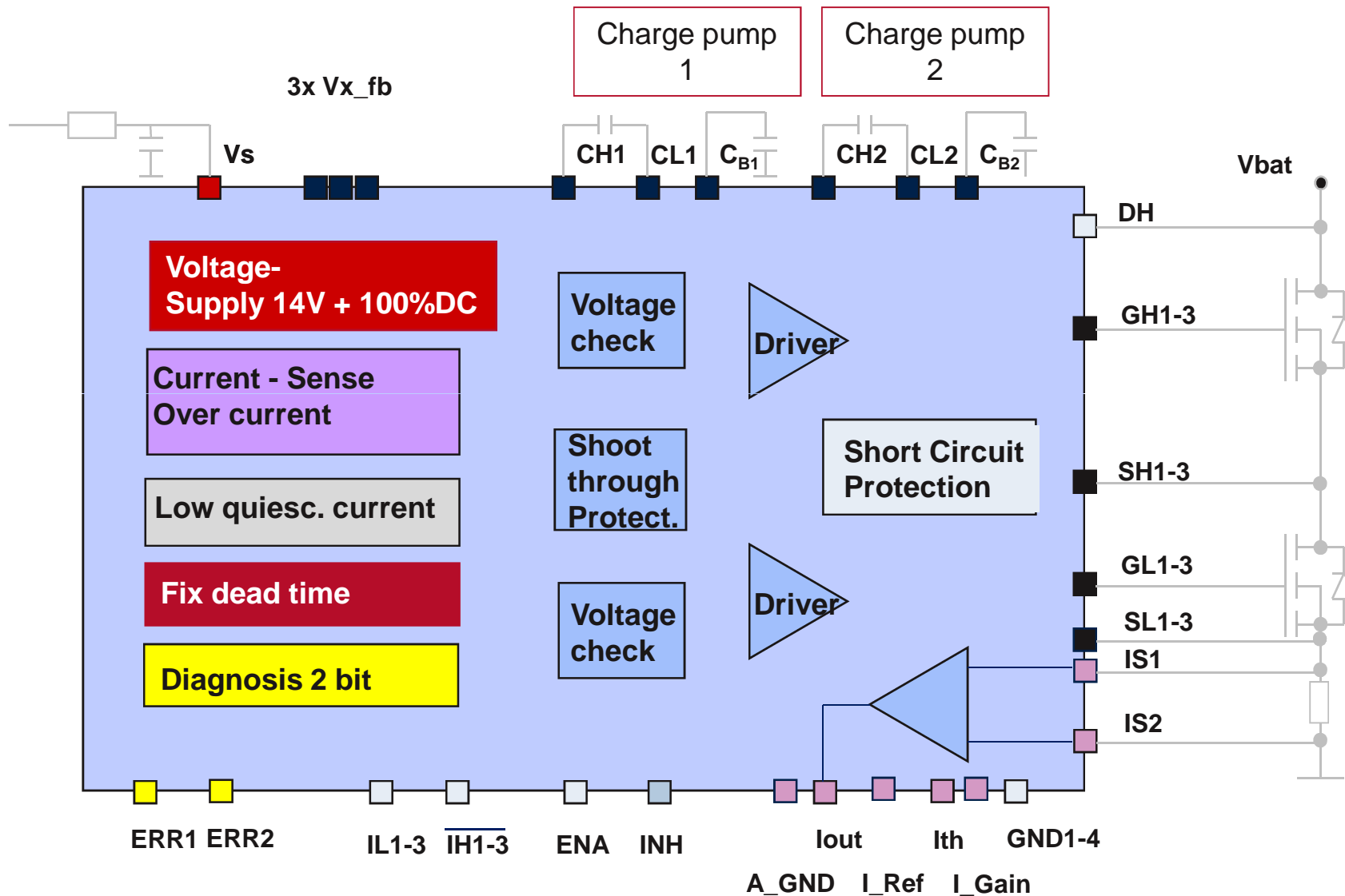

# TLE718x 3-Phase Driver IC for 12V

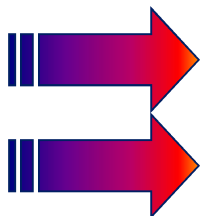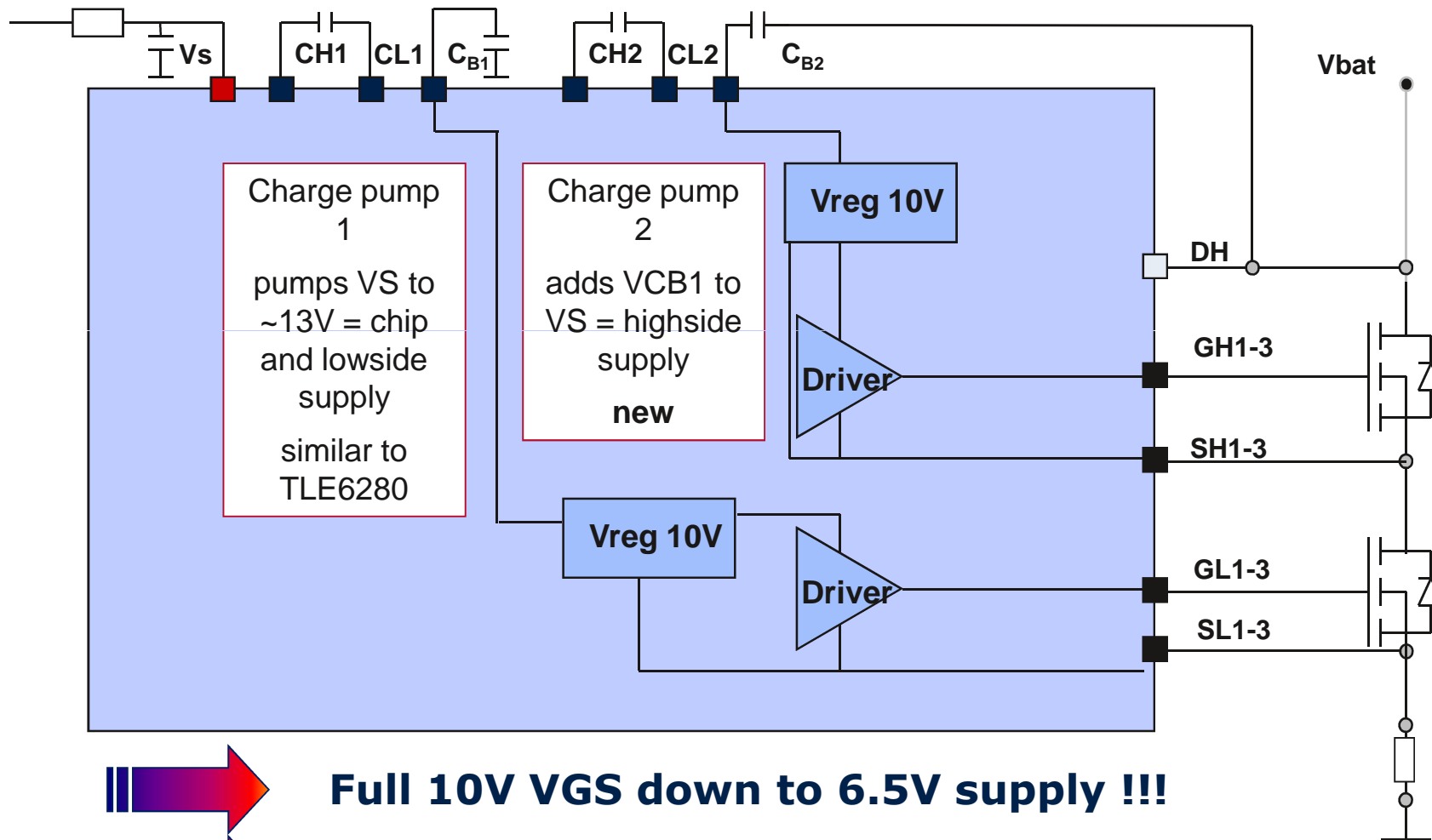

**Full 10V VGS down to 6.5V supply !!!**

**0 – 100% without limits**

# TLE718x

## Gate voltages at low supply voltages

For internal use only!



### Conditions:


$V_S = 5.5 \dots 12 \text{ V}$

$Q_G = 130 \text{ nC}$

$f = 20 \text{ kHz}$

(Max. UV limit on CB1: 8.3 V)

0...100% duty cycle

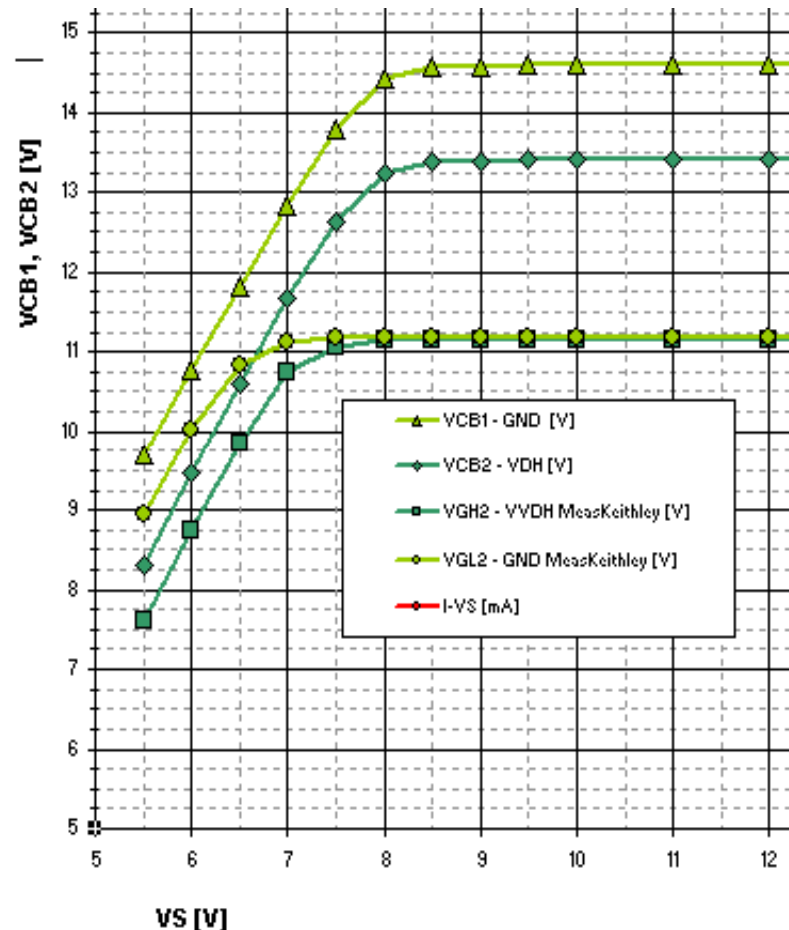


full supply voltage reaches motor



highest efficient usage of motor (costs + space)

# TLE7189

## 3-Phase Driver IC for 12V

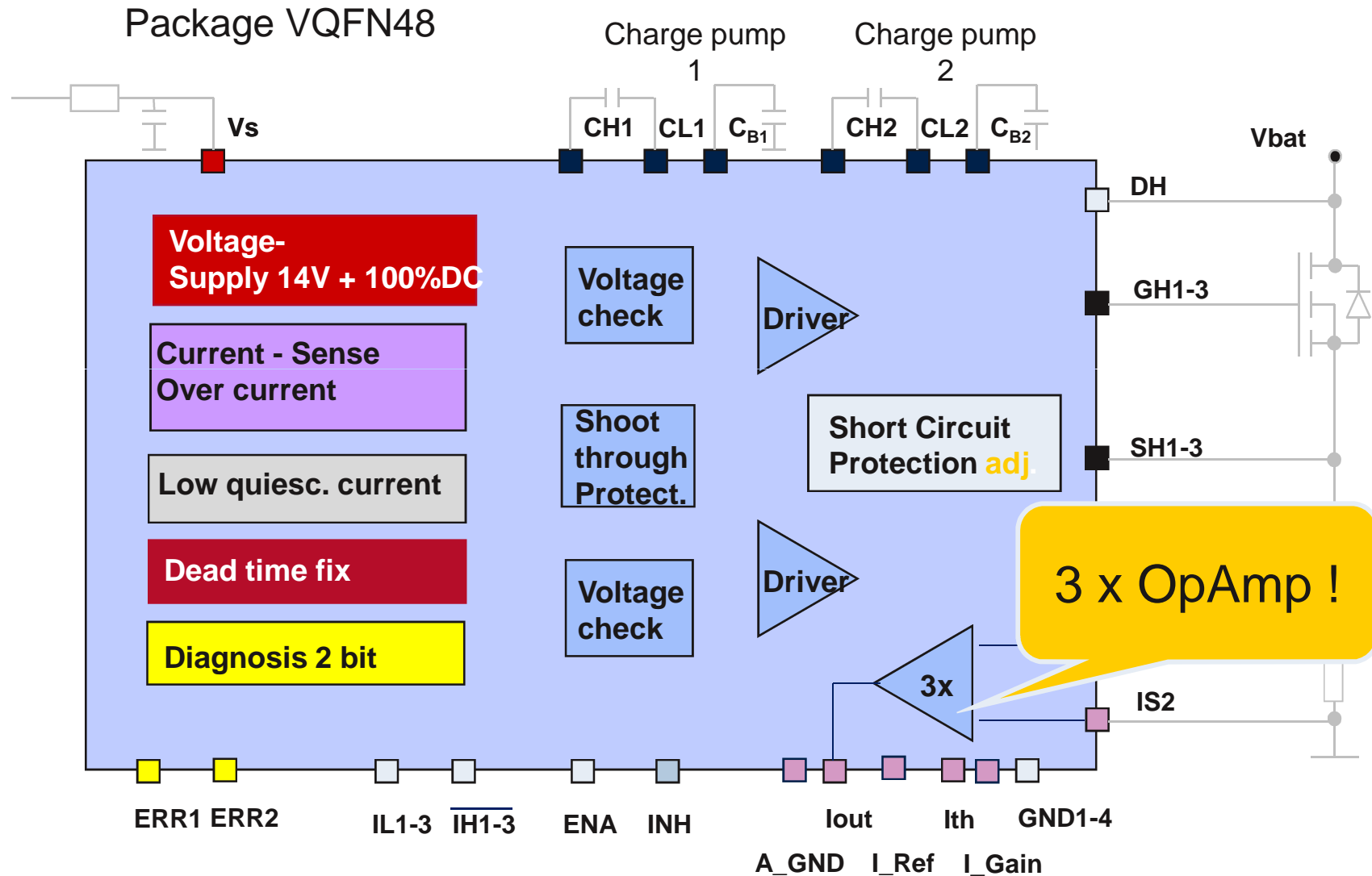

# TLE7185

## Simplified 3-phase driver IC



low cost

### ■ Features

#### ■ B6 MOS Bridge driver

- ☐ ~10 Ohm output stages for MOSFETs up to 100A (300mA Gate current)
- ☐ 0-95% duty cycle (bootstrap principle)
- ☐ Adj. Short circuit detection level 0.3-2V
- ☐ Adj. Dead time
- ☐ Low quiescent current mode 20uA
- ☐ 2 bit diagnostic
- ☐ Separate Source pin for each MOSFET
- ☐ Functional range 5.5 to 33V

#### ■ Charge pump to boost the supply voltage


#### ■ P-DSO36-Exposed pad allows TA up to 140°C



**Optimized for applications running  
at 5.5V supply**

# BLDC Drive for Fans and pumps (and EPS) TLE7184

  
In Production

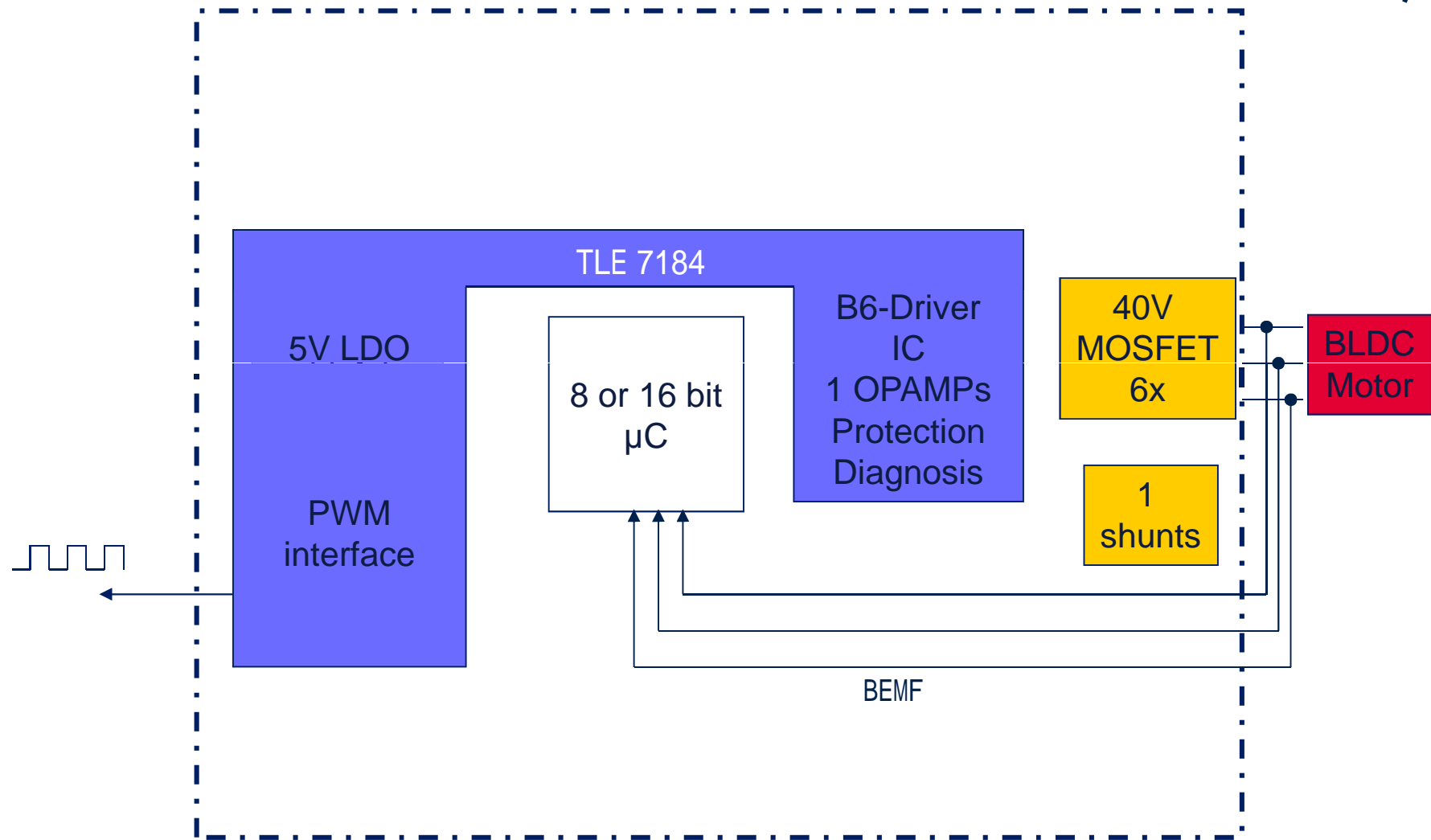



# BLDC Drives

## ASSP- Approach TLE7184



low cost

### ■ Features

#### ■ B6 MOS Bridge driver

- ~10 Ohm output stages for MOSFETs up to 100A
- Works down to 7V
- OpAmp (UGBW 20Mhz / <1.5mV)
- 0-94% duty cycle (bootstrap principle)
- Protection functions

#### ■ 5 or 3.3V 70mA LDO to support 8 and 16bit uCs

#### ■ PWM interface

#### ■ Precise analog and digital temperature sense

#### ■ Specific Logic

#### ■ VDH switch (disconnects circuit from battery – sleep mode)



**Simplified ECU for BLDC Motors**



**Lowest cost approach for EPS**

# Agenda

## ■ Application requirements EPS (**P**ermanent **M**agnet **S**ynchronous **M**otor)

### □ Driving high currents

- ▢ Spikes: Why they are harmful
- ▢ Layout recommendations
- ▢ Requirements to MOSFETs and Driver ICs

### □ Measure Current precisely


- ▢ How many shunts to use?
- ▢ How does it work with one shunt
- ▢ Requirements for driver IC
- ▢ What to consider with IFX OpAmps in driver ICs

### □ Functional Safety: Second switch off path

- ▢ Star-Point relay vs. MOSFETs

# Application trends

## Current measurement

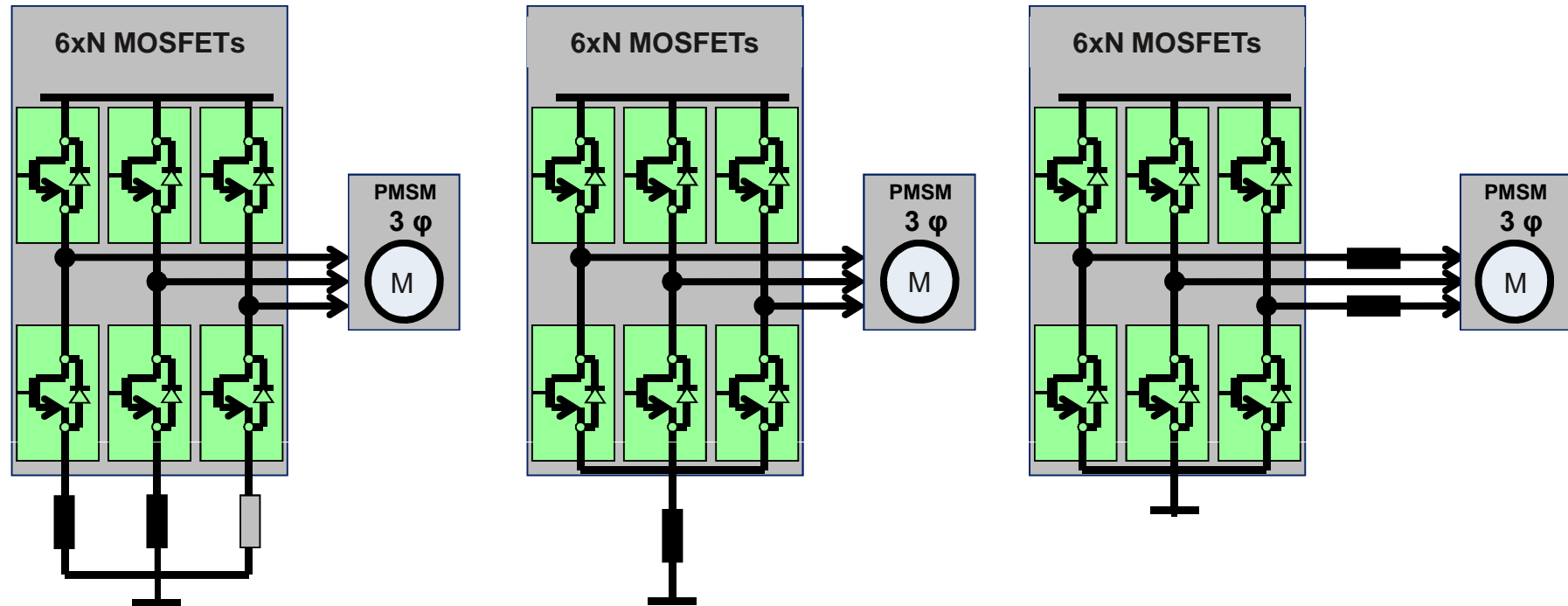

### ■ Options

- ☐ 2 or 3 shunts at the Source of the MOSFETs
- ☐ Single shunt in common GND
- ☐ 2 shunts in phase

☐ ...

# Bridge Driver ICs -Electric Power Steering

## Features overview



Shunt configurations	2 shunts @ Sources of low side MOSFETS	3 shunts @ Sources of low side MOSFETS	1 shunt in common GND	2 shunts in the phase connections
Costs	0	-	+	-
Power Dissipations	-	--	+	--
Space	-	--	+	-
Easy to measure	+	++	0	- (common mode )
Redundancy	-	Yes	-	-
Verification of measurement	against motor model	directly	against motor model	against motor model
Supported by IFX driver ICs	TLE7189	TLE7189	TLE7183 / 84 / 86	No



■ Europe : 1 shunt in GND / 2 shunts @ source

■ Japan: Often 3 shunts in GND

# How to measure with 1 shunt

## Short times to measure


### ■ Example center aligned PWM

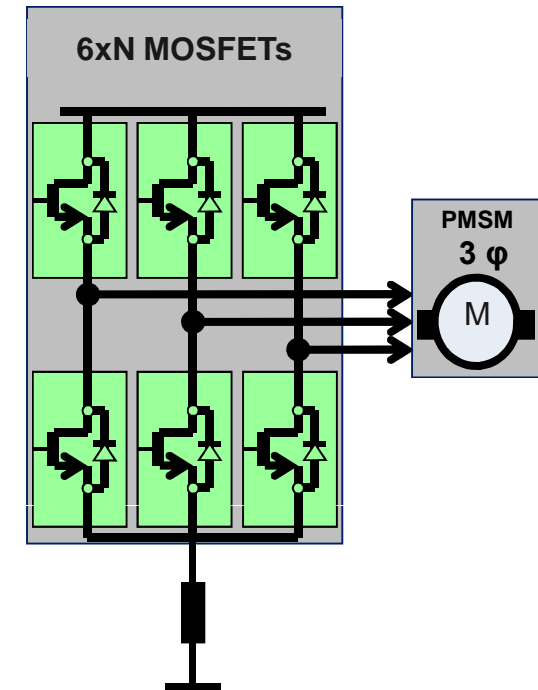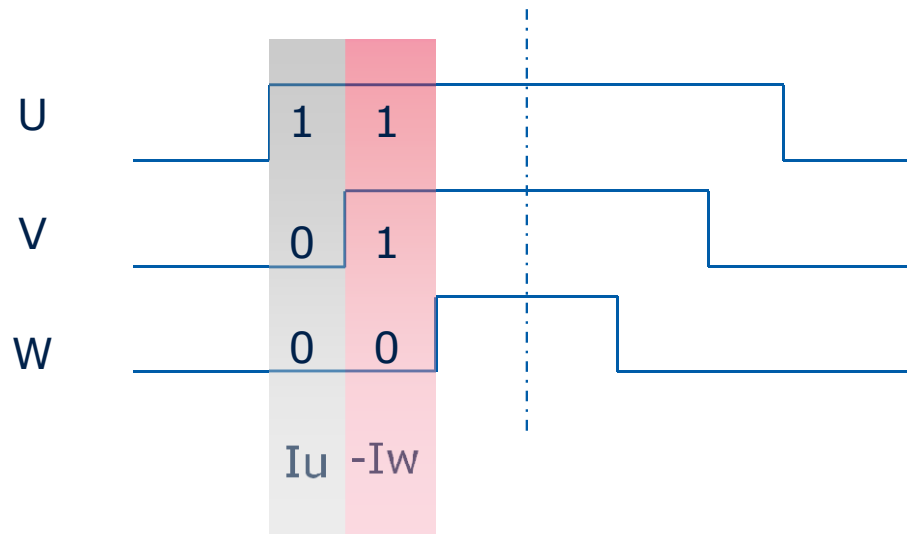

- 2 phase currents can be measured
- 3<sup>rd</sup> phase current can be calculated

# How to measure with 1 shunt

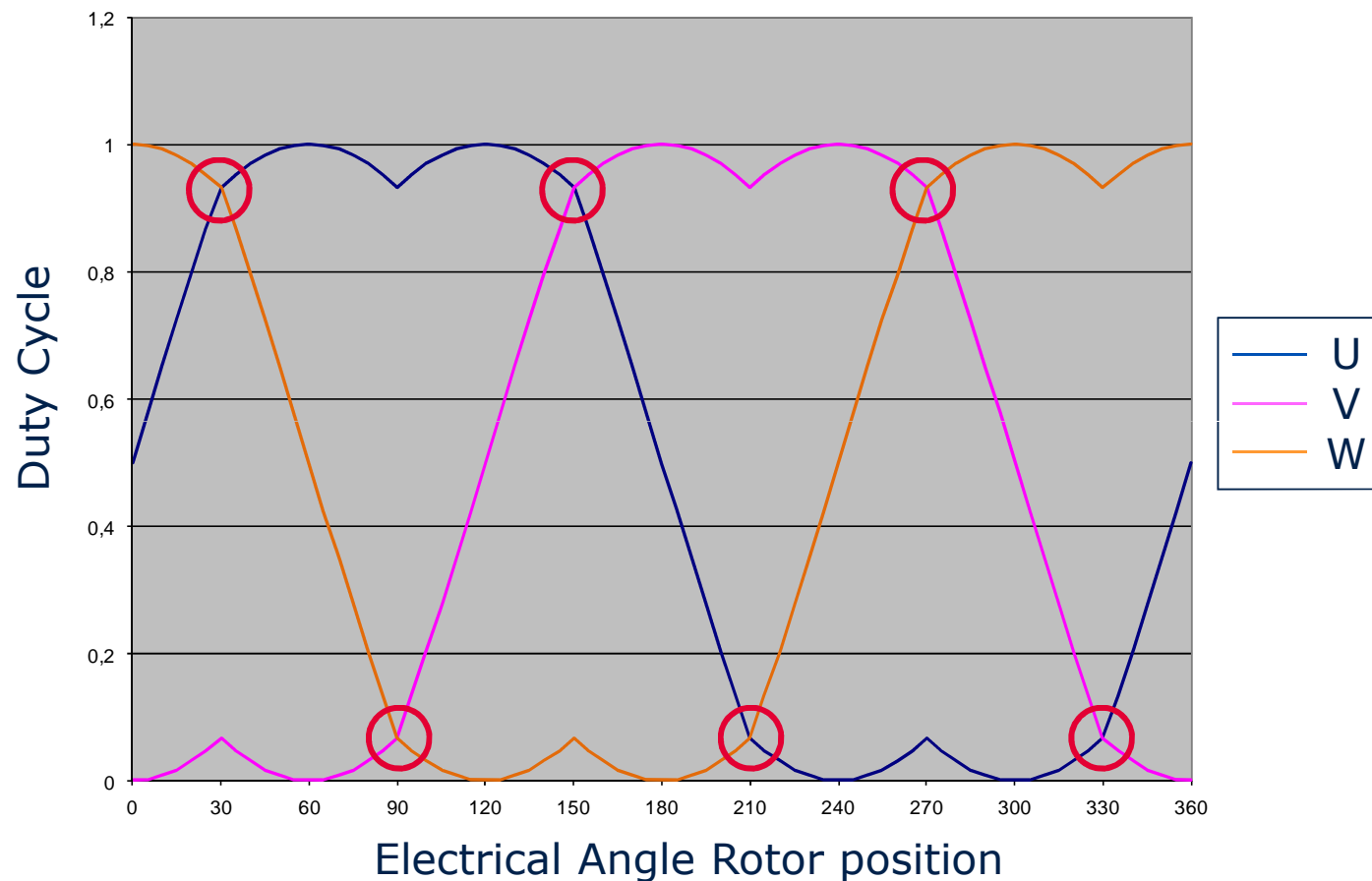
## Problem Zones @ space vector modulation




■ Only one current can be measured
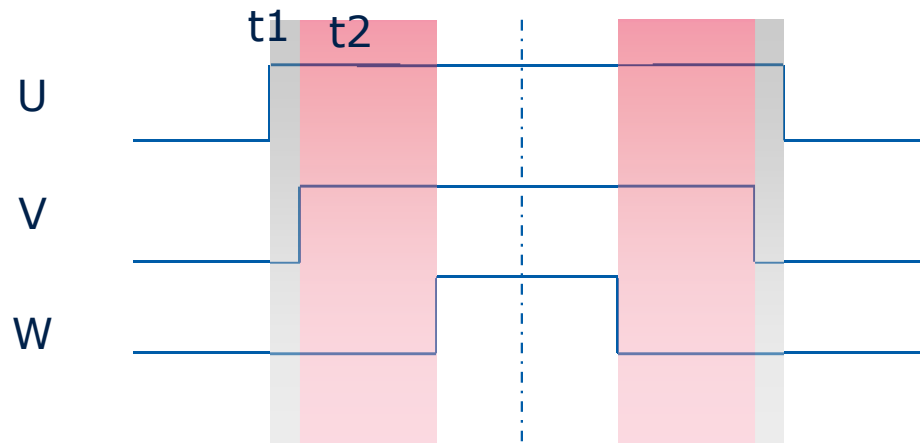
# Work around Short times to measure

- t1 is too short do measure current -> dt helps


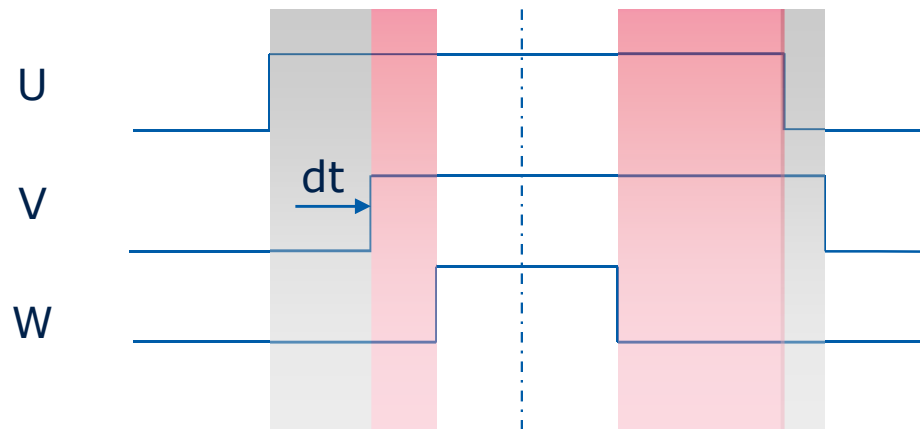
$$2 * t_1 * \begin{pmatrix} 1 \\ 0 \\ 0 \end{pmatrix} + (2 * t_2) * \begin{pmatrix} 1 \\ 1 \\ 0 \end{pmatrix} = \begin{pmatrix} 2 * t_1 + 2 * t_2 \\ 2 * t_2 \\ 0 \end{pmatrix}$$



$$(t_1 + dt) * \begin{pmatrix} 1 \\ 0 \\ 0 \end{pmatrix} + (t_2 - dt) * \begin{pmatrix} 1 \\ 1 \\ 0 \end{pmatrix} + (t_2 + t_1) * \begin{pmatrix} 1 \\ 1 \\ 0 \end{pmatrix} + (dt - t_1) * \begin{pmatrix} 0 \\ 1 \\ 0 \end{pmatrix} =$$

$$\begin{pmatrix} t_1 + dt + t_2 - dt + t_2 + t_1 \\ t_2 - dt + t_2 + t_1 + dt - t_1 \\ 0 \end{pmatrix} = \begin{pmatrix} 2 * t_1 + 2 * t_2 \\ 2 * t_2 \\ 0 \end{pmatrix}$$

- Motor sees the same vector!

# Application requirements Power Steering

## ■ Current measurement

- Only one shunt for cost reasons
- very short time to measure current
- increasing accuracy requirements
- high current in application lead to negative spikes at shunt

## ■ OpAmp requirements



- input range +/-5V spikes 4
- high bandwidth typ. 20 MHz UGBW
- low input offset down to +/- 1.5mV
- high CMRR > 60db minimum



**TLE7183 / 89 / 84 / 86**

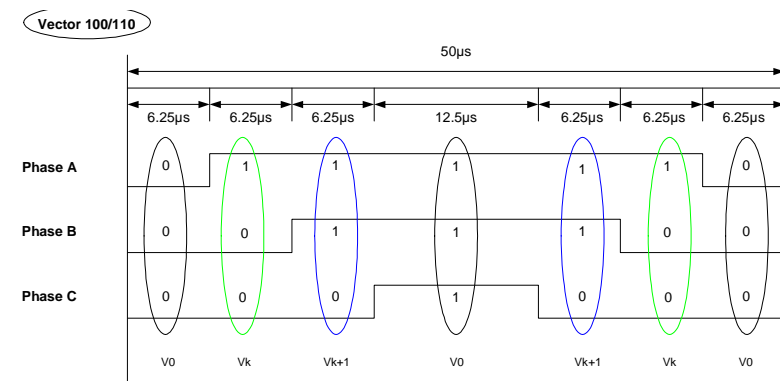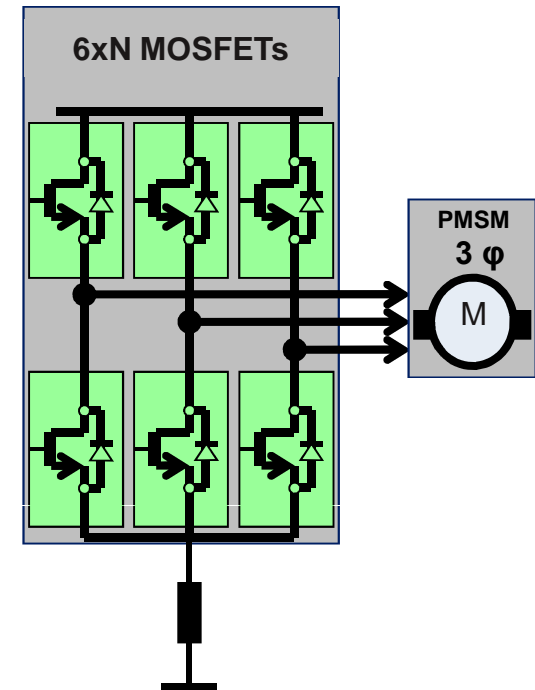26.09.2011

Copyright © Infineon Technologies 2011. All rights reserved.






# TLE7189F 3-Phase Driver IC for 12V


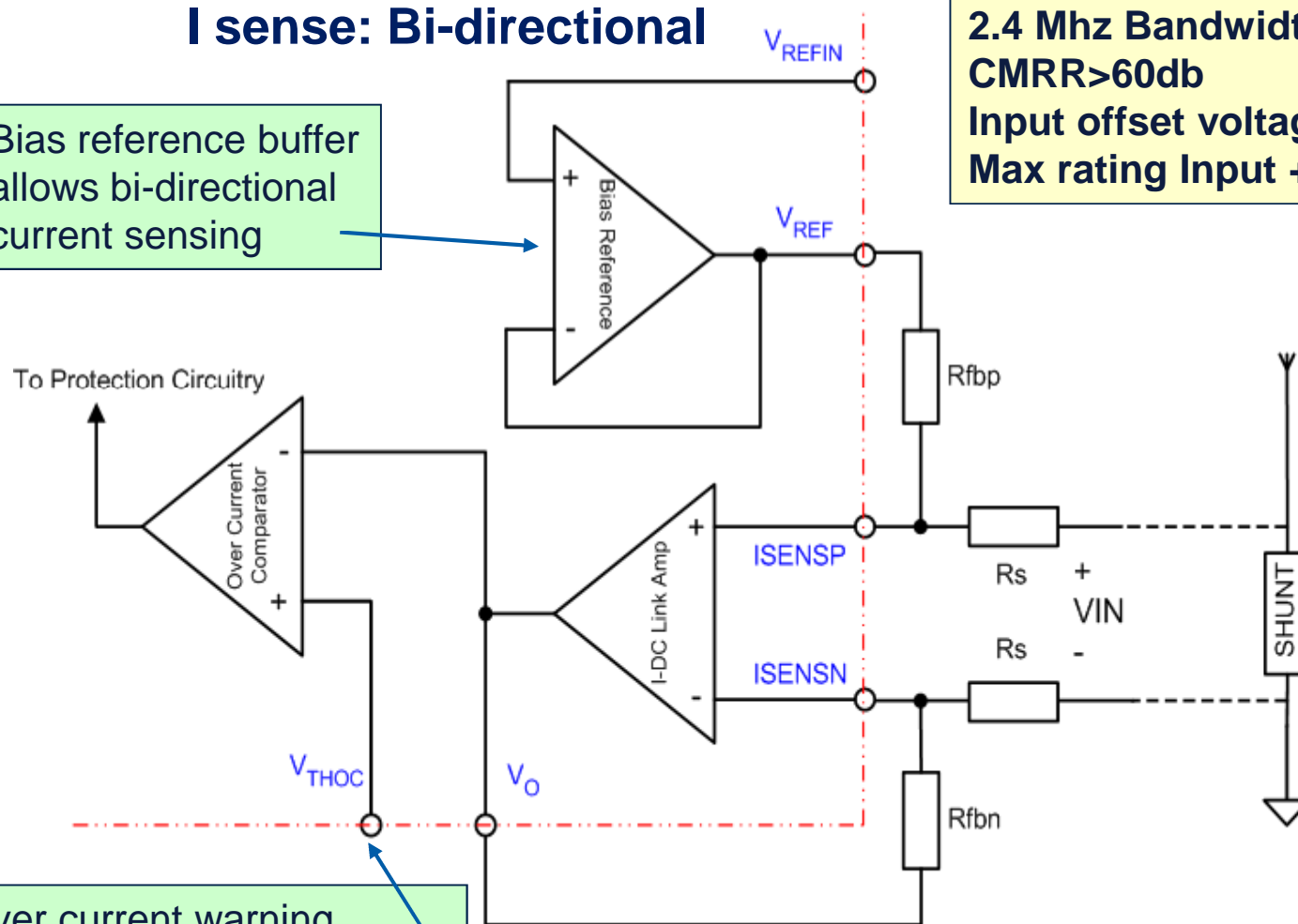
## I sense: Bi-directional

Bias reference buffer allows bi-directional current sensing



2.4 Mhz Bandwidth @ gain 15  
CMRR>60db  
Input offset voltage <+/-1.5mV  
Max rating Input +/-5V

Over current warning with adjust. Current level

# Agenda

## ■ Application requirements EPS (**P**ermanent **M**agnet **S**ynchronous **M**otor)

### □ Driving high currents

- └ Spikes: Why they are harmful
- └ Layout recommendations
- └ Requirements to MOSFETs and Driver ICs

### □ Measure Current precisely

- └ How many shunts to use?
- └ How does it work with one shunt
- └ Requirements for driver IC
- └ What to consider with IFX OpAmps in driver ICs

### □ Functional Safety: Second switch off path

- └ Star-Point relay vs. MOSFETs


# EPS relay removal

Normally  
Replaced by fuse (and  
reverse polarity MOSFET)

OEMs try to remove this

Vbatt Relay

Starpoint Relay

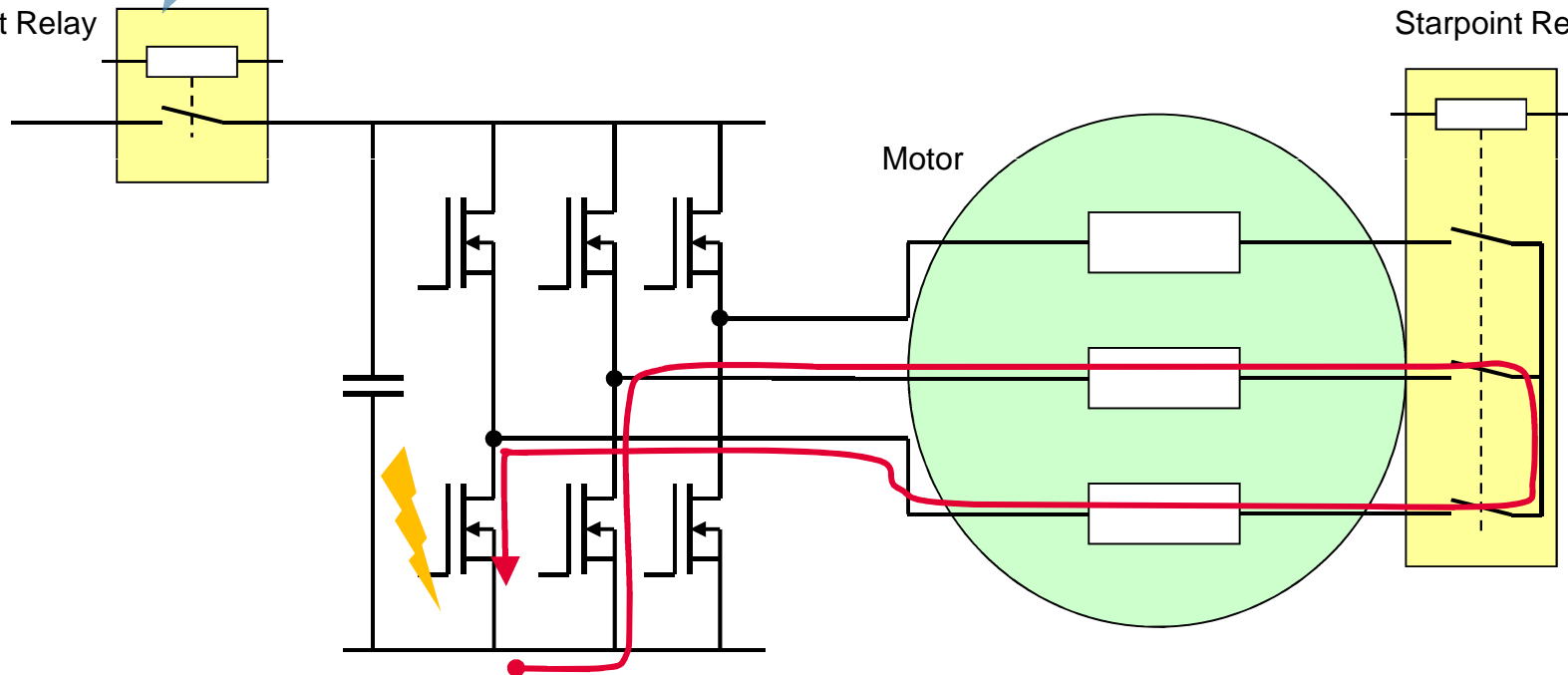

Task of starpoint relay @ PMSM : Avoid currents like shown to avoid breaking

# EPS relay removal



## Product Features (Please use the Product Drawing for all design activities)

### Product Type Features:



- Product Designation = High Current Solutions
- Series = V23135

### Electrical Characteristics:

- Nominal Voltage (VDC) = 12
- Rated Current @ 85° C (A) = 90
- Coil Resistance ( $\Omega$ ) = 150
- High Power Relays >75A = Yes
- Contact - Switching Current Min. (mA) = 1000
- Contact - Switching Voltage Max. (VDC) = See Load Limit Curve
- Coil - Rated Power (W) = 0.96
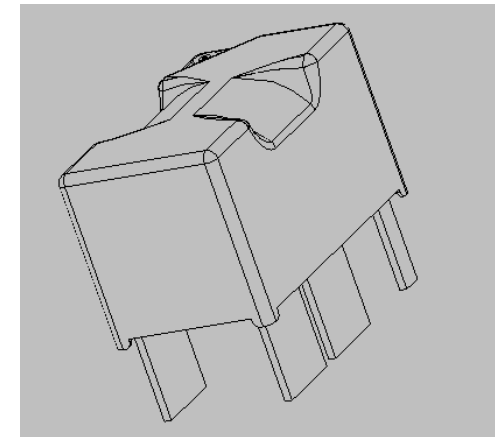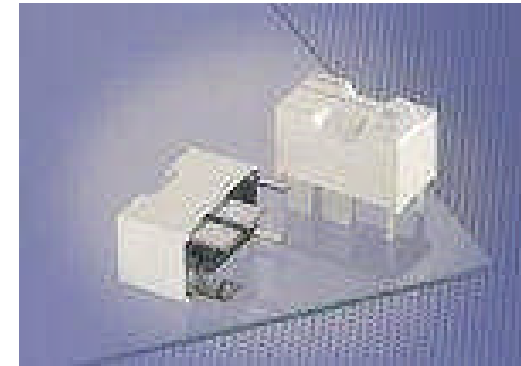
### Body Features:

- Mounting Bracket(s) = Without
- Length (mm [in]) = 32.30 [1.272]
- Width (mm [in]) = 18.30 [0.720]
- Height (mm [in]) = 18.70 [0.736]
- Weight (g [oz]) = 30.00 [1.058]




## ■ Remove why?

- ☐ Too big
- ☐ Too expensive
- ☐ Not robust enough (produces fails over lifetimes)
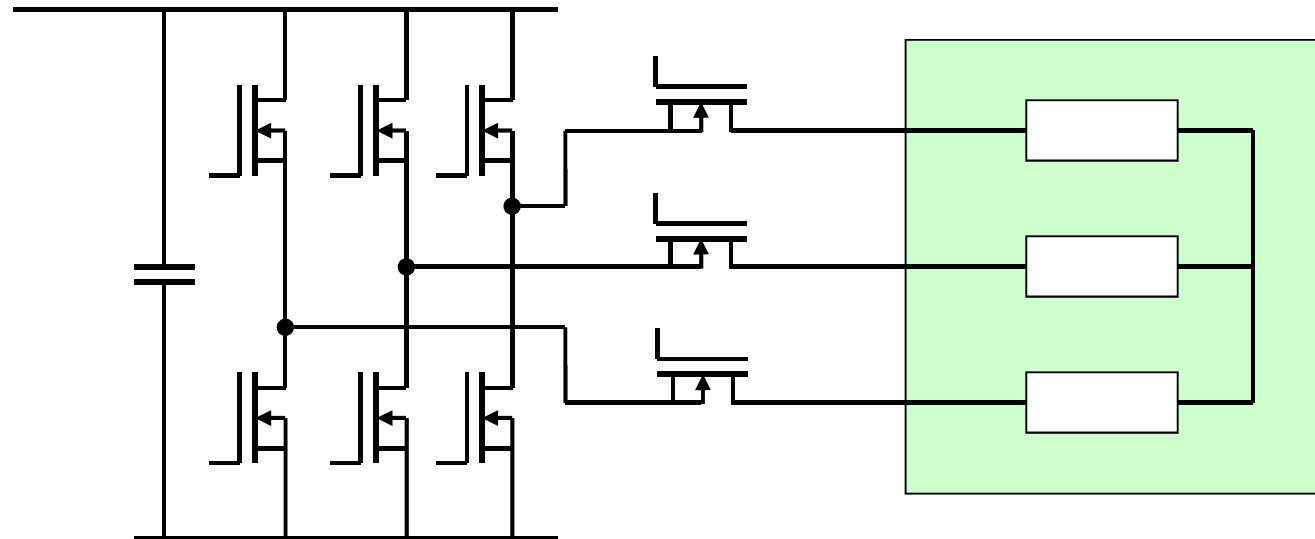
## ■ Alternative


- Use MOSFETs to disconnect phases
- But: In emergency case no freewheeling path
- High avalanche robustness of MOSFET required
- Or: Intelligent MOSFET switch off strategy
- Charge pump of driver can be used for supply




# EPS relay removal

- But be careful
- Many patents around
- E.g.:

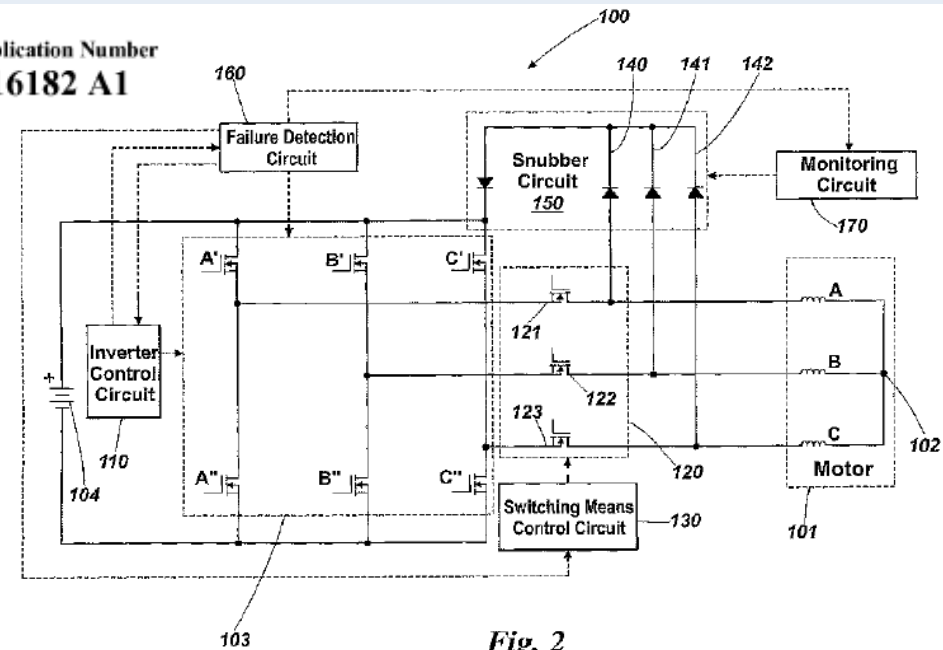(10) International Publication Number  
WO 2010/116182 A1



(10) Patent No.: US 7,019,479 B2

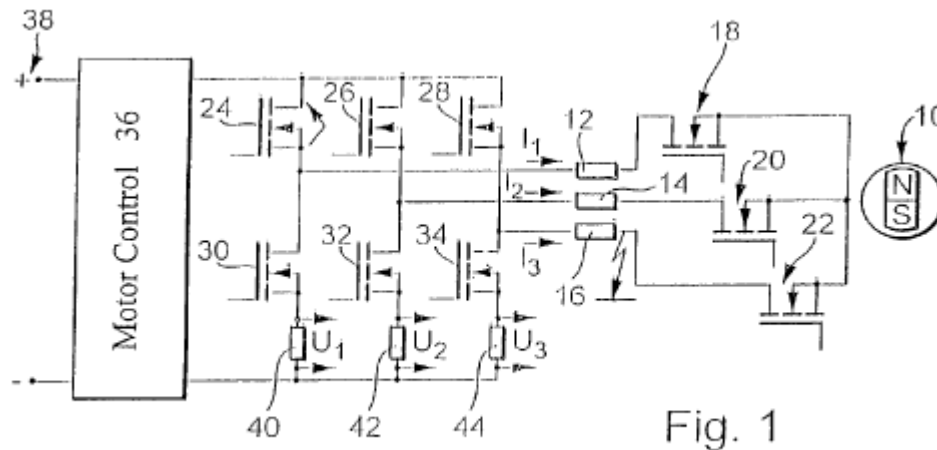


# TLE 7189

## SIL 3 supporting features



**“Single failure does not cause short in bridge or motor operation”**

FTA for TLE7189 proves:

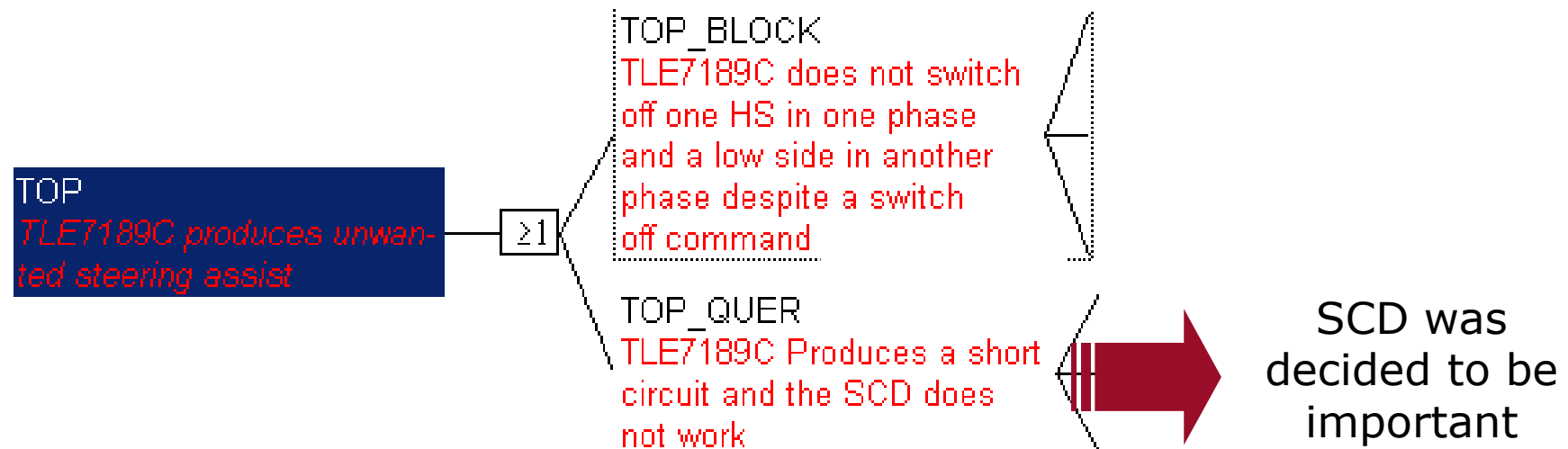



## Philosophy

**Use TLE718X and add SIL3 related supervision:  
"sleeping bug is excluded by repeated testing"**

- ⇒ **VCC check (monitors the uC supply)**
- ⇒ **Test function for VCC check**
  
- ⇒ **SC-Detection (monitors short circuit of MOSFET)**
- ⇒ **Test function for SC-Detection at 0A**
  
- ⇒ **High voltage inputs (18V)**
  
- ⇒ **"Common mode failure analysis" (FTA) available, tailored to the FMEA and the FTA of the target system**



# Electric Power Steering Requirements vs Products



TLE7189

TLE7183

TLE7185

TLE7184/6

## ■ 160A B6-Bridge

- powerful output stage
- Robust to spikes
- Separate Source connections
- Floating output stages

4

4

4

4

4

4

4

4

4

4

4

4

4

4

4

4

## ■ Highest efficiency (0-100%dc)

4

4

low cost

low cost

## ■ OpAmp requirements

- input range +/-5V spikes
- high bandwidth
- low input offset
- high CMRR

4

4

4

4

4

4

4

~

4

4

4

4

## ■ Functional Safety Features

4

4

## ■ Integrated 5 or 3.3V Vreg

<70mA

A background image showing a person in a white cleanroom suit and mask working in a laboratory or cleanroom environment. The person is holding a small object, possibly a component, and is looking down at it. The background is slightly blurred, showing other equipment and the cleanroom environment.

**We commit.**  
**We innovate.**  
**We partner.**  
**We create value.**